

amateur radio

Vol. 36, No. 12

DECEMBER 1968

Registered at G.P.O., Melbourne, for
transmission by post as a periodical

Merry Christmas and Happy New Year to all our Clients

FIXED CONDENSERS

125 Volt Rating:

10, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 220, 270, 330, 390, 425, 470, 560 pF. all 15c ea.

0.01 uF.	160v.	12c	0.0018 uF.	600v.	18c
0.01	600v.	25c	0.0022 uF.	600v.	12c
0.012	125v.	13c	0.0022 uF.	600v.	18c
0.012	400v.	12c	0.0027 uF.	400v.	17c
0.012	600v.	18c	0.0027 uF.	600v.	18c
0.015	125v.	13c	0.0033 uF.	400v.	12c
0.015	600v.	18c	0.0033 uF.	600v.	14c
0.018	600v.	22c	0.0039 uF.	400v.	12c
0.022	125v.	13c	0.0039 uF.	600v.	18c
0.022	400v.	14c	0.0047 uF.	400v.	15c
0.022	600v.	24c	0.0047 uF.	600v.	22c
0.027	150v.	14c	0.0056 uF.	400v.	15c
0.027	400v.	15c	0.0056 uF.	600v.	13c
0.027	600v.	22c	0.0068 uF.	400v.	15c
0.033	125v.	14c	0.0068 uF.	600v.	15c
0.033	600v.	15c	0.1	125v.	15c
0.033	600v.	22c	0.1	400v.	18c
0.039	125v.	14c	0.1	600v.	27c
0.039	600v.	18c	0.2	400v.	20c
0.039	600v.	28c	0.5	400v.	20c
0.047	125v.	14c	0.12	125v.	25c
0.047	400v.	14c	0.12	600v.	20c
0.047	400v.	14c	0.15	125v.	15c
0.056	125v.	14c	0.15	400v.	15c
0.056	400v.	14c	0.15	600v.	20c
0.056	600v.	18c	0.18	125v.	17c
0.056	600v.	18c	0.18	400v.	17c
0.068	400v.	14c	0.22	125v.	15c
0.068	600v.	18c	0.22	400v.	22c
0.068	600v.	20c	0.22	600v.	24c
0.082	400v.	22c	0.27	125v.	22c
0.082	600v.	28c	0.27	400v.	25c
0.082	600v.	28c	0.27	600v.	28c
0.001	125v.	15c	0.33	125v.	25c
0.001	400v.	15c	0.33	400v.	28c
0.001	600v.	18c	0.33	600v.	28c
0.001	5Kv.	45c	0.39	160v.	22c
0.001	Feet.	125v.	0.39	160v.	22c
0.0012 uF.	400v.	15c	0.47	125v.	28v
0.0012	600v.	15c	0.47	400v.	35c
0.0015	250v.	15c	0.47	600v.	40c
0.0015	600v.	15c	0.68	125v.	35c

MULTIMETER, Model OL-64

20,000 ohms per volt d.c., 8,000 ohms per volt a.c.

Specifications:

D.C. volts: 0-0.1, 1, 10, 50, 250, 500, 1,000, 5,000.
A.C. volts: 0-10, 50, 250, 1,000.
D.C. current: 0-30 uA, 1, 50, 500 mA; 10 A.
Resistance: 0.5, 500K ohms, 5, 50 megohms.
Decibels: Minus 20 to plus 22 db., plus 20 to plus 30 db.
Capacitance: 250 pF. to 0.02 uF.
Inductance: 0-5000 H.
Load current: 0-1.00, 0.6, 60 mA.
Self contained batteries: 22.5v. (8L-015) x 1, 1.5v. (UM3) x 2.
Size and weight: 6 x 4-1/5 x 2 in, 650 g.
Meter movement: full sensitivity: 30 uA., F.S.D.
Price \$19.75, postage 25c.

CRYSTAL MICROPHONES

Price only
\$5.50



Packing and Postage 25c.
Model BM3 (illustrated): Response 100-8,000 cycles, fitted with 6 ft. cable and phone plug with on-off switch. Can be used on stand or for hand use.
BM3 Insert, \$1.00 each

ALARM BELLS

(Parachute type), 6 volt. Suitable for Burglar Alarm, etc., complete with trip rope, etc. Price \$1.25, post 50c.

SCOOP PURCHASE!

1/2W. AND 1W. RESISTORS

Cracked Carbon 5%, Preferred Range:

10, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1.2K, 1.5K, 1.8K, 2.2K, 2.7K, 3.3K, 3.9K, 4.7K, 5.6K, 6.8K, 8.2K, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M, 2.2M, 3.3M, 3.9M, 4.7M, 5.6M, 6.8M, 8.2M, 10M.

1/2 watt: 8c ea. or \$6.00 per 100
1 watt: 10c ea. or \$7.00 per 100
When ordering 100 or over, minimum quantity of 10 of each selected type.

STEREO HEADPHONES

Large rubber eartips, full audible frequency.
50-1500 cycles. Price \$9.00.

MULTIMETER, Model 200H

20,000 ohms per volt d.c., 10,000 ohms per volt a.c.

Specifications:

D.C. volts: 0-5, 25, 50, 250, 500, 2500.
A.C. volts: 0-10, 50, 100, 500, 1000.
D.C. current: 0-50 uA; 25, 250 mA.
Resistance: 0-50,000 ohms; 0-6 meg.
Capacity: 0.01-0.3 uF (at A.C. 5v.).
0.0001-0.01 uF (at A.C. 250v.).
Decibel: Minus 20 db., plus 22 db.
Output range: 0-10, 50, 100, 500, 1000.
Battery used: UM3 1.5v., 1-piece.
Dimensions: 3 1/4 x 4 1/2 x 1 1/2 inch.
Price \$11.25, inc. tax, post free.
Complete with internal battery, testing leads, prods.



BARGAINS!!

Philips Trimmers 10-60 pF, 32c; 3-30 pF, 23c
NE2 Neon Tubes 90v, 30c; 240v, 50c
Bezel Lamp Holders and Globe, red/white 45c ea.
Banana Plugs and Sockets 12c ea.
FT243 Crystal Sockets 29c ea.
Don Miniature Crystal Sockets 29c ea.
HC18 Crystal Sockets 40c ea.
Transistor Plugs and Sockets, 3.3m. 35c pr.
P.M.G. Plugs 40c ea.
P.M.G. Sockets 35c ea.
P.M.G. Joiner Socket 75c ea.
Dim Plugs, Single Pin 25c ea.
Dim Plugs, Three Pin 45c ea.
Dim Plugs, Five Pin 45c ea.
Dim Plug Joiners, Three and Five Pin 45c ea.
Coil Formers, 1 1/4 inch diam., available in 100 and five pin bases 35c ea.
2.5 mH. R.F. Chokes 48c ea.
Erg Insulators 8c ea.
Speaker Plugs and Socket, four pin 18c ea.
Apele Coils, STC 51c ea.
" " M26A 32.50 ea.
" " S0515 51.50 ea.
" " S203 51.50 ea.

BARGAINS!!

100-60 pF, 32c; 3-30 pF, 23c
NE2 Neon Tubes 90v, 30c; 240v, 50c
Bezel Lamp Holders and Globe, red/white 45c ea.
Banana Plugs and Sockets 12c ea.
FT243 Crystal Sockets 29c ea.
Don Miniature Crystal Sockets 29c ea.
HC18 Crystal Sockets 40c ea.
Transistor Plugs and Sockets, 3.3m. 35c pr.
P.M.G. Plugs 40c ea.
P.M.G. Sockets 35c ea.
P.M.G. Joiner Socket 75c ea.
Dim Plugs, Single Pin 25c ea.
Dim Plugs, Three Pin 45c ea.
Dim Plugs, Five Pin 45c ea.
Dim Plug Joiners, Three and Five Pin 45c ea.
Coil Formers, 1 1/4 inch diam., available in 100 and five pin bases 35c ea.
2.5 mH. R.F. Chokes 48c ea.
Erg Insulators 8c ea.
Speaker Plugs and Socket, four pin 18c ea.
Apele Coils, STC 51c ea.
" " M26A 32.50 ea.
" " S0515 51.50 ea.
" " S203 51.50 ea.

SPECIAL! BARGAIN PRICES!

RECORDING TAPES

Well known make, fully guaranteed, sealed cartons

		3 INCH SPOOLS	
150 Feet	Acetate Base	55c
225 Feet	Acetate Base	75c
300 Feet	Mylar Base	\$1.15
		3 1/4 INCH REELS	
600 Feet	Mylar Base	\$1.85
		4 INCH REELS	
400 Feet	Acetate Base	\$1.40
		5 INCH REELS	
600 Feet	Acetate Base	\$1.85
900 Feet	Acetate Base	\$2.30
900 Feet	Mylar Base	\$3.00
1200 Feet	Mylar Base	\$3.80
1800 Feet	Mylar Base	\$5.75
		5 1/4 INCH REELS	
900 Feet	Acetate Base	\$2.45
1200 Feet	Acetate Base	\$3.40
1200 Feet	Mylar Base	\$3.75
1800 Feet	Tensilised Mylar Base	\$4.75
		7 INCH REELS	
1200 Feet	Acetate Base	\$3.00
1200 Feet	Mylar Base	\$3.75
1800 Feet	Acetate Base	\$4.50
1800 Feet	Mylar Base	\$5.00
2400 Feet	Mylar Base	\$6.25
3600 Feet	Mylar Base	\$9.75
		EMPTY REELS	
3 inch 25c	5 inch 40c
3 1/4 inch 35c	5 1/4 inch 55c
4 inch 40c	7 inch 50c
Postage 20c.			

POWER TRANSFORMERS

VOLTAGE DOUBLER TYPES

Type	H.T. Sec.	Max. Volts	Heater D.C. mA	Winding V. A.	Price
PT2062	115	80	6.3CT	2.25	\$16.80
PT2063	tap 105	80	6.3CT	2.25	\$13.40
PT2067	tap 125	100	6.3CT	4	\$12.00
PT2064	taps 110, 100	125	6.3	2.25	\$12.30
PT2065	tap 125	150	6.3CT	2.25	\$13.60
PT2066	tap 105	150	6.3CT	3	\$12.20
PT2068	115	190	6.3CT	3	\$13.70
PT1965	taps 185, 175	200	6.3	4	\$21.00
	115	300	6.3CT	3	\$29.00

FULL WAVE TYPES—VALVE RECTIFIER

Type	H.T. Sec.	Max. Volts	Rectifier D.C. mA	Heater V. A.	Other Heaters V. A.	Price
PT1992	150-0-150	30	6.3	1.7		\$5.00
PT1951	180-0-180	60	6.3	2		\$6.70
PT1940	285-0-285	40	6.3	2		\$6.30
	tap 5 2		6.3	2		\$5.70
PT1993	225-0-225	50	6.3	2		\$5.70
PT1941	285-0-285	60	6.3	2		\$9.60
	tap 5 2		6.3	2		\$9.60

S.W.R. METERS, MODEL KSW-10

Specifications—Standing Wave Ratio: 1:1 to 1:10.
Accuracy: Plus or minus 3 per cent, scale length.
Impedance: 50 ohms and 75 ohms. Meter: 0-100 DC microamperes. Price \$19 inc. tax.

STEP-DOWN TRANSFORMERS

Primary: 240 volts. Secondary (switched): 24, 28 or 32 volts a.c., 50 cycle, 1.88 amp., with on/off switch and two outlet sockets. \$7.00, post \$1.00.

HAM RADIO SUPPLIERS

323 ELIZABETH STREET, MELBOURNE, VIC., 3000

Phones: 67-7329, 67-4286 All Mail to be addressed to above address

amateur radio

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA FOUNDED 1910



DECEMBER 1968
Vol. 36, No. 12

Editor:

K. E. PINCOTT VK3AFJ

Assistant Editor:

E. C. Manifold VK3EM

Publications Committee:

G. W. Bate (Secretary) VK3AOM

A. W. Chandler (Circulation) VK3LC

Ken Gillespie VK3GK

Draughtsmen:

Clare Allan VK3ZIV

Peter Ramsay VK3ZWN

Ian Smith 36 Green St., Noble Park

Advertising Enquiries:

C/o. P.O. Box 36, East Melbourne, Vic., 3002.

or
Mrs. BELLAIRS, Phone 41-3535, 478 Victoria

Parade, East Melbourne, Vic., 3002. Hours:

10 a.m. to 3 p.m. only.

Advertising copy (except Hamads) should be forwarded direct to the printers by first of each month.

Publishers:

VICTORIAN DIVISION W.I.A.

Reg. Office: 478 Victoria Parade, East Melbourne, Vic., 3002.

Printers:

"RICHMOND CHRONICLE," Phone 42-2419.

Shakespeare Street, Richmond, Vic., 3121.



All matters pertaining to "A.R." other than subscriptions, should be addressed to:

THE EDITOR,

"AMATEUR RADIO,"

P.O. BOX 36,

EAST MELBOURNE, VIC., 3002.

Acknowledgments will be sent following the Committee meeting on the second Monday of each month. All Sub-Editors should forward their articles to reach "A.R." before the 5th of each month. Any item received after the Committee meeting will be held over until the next month. Publication of any item is dependent upon space availability, but in general about two months may elapse before a technical article is published after consideration by the Publications Committee.



Members of the W.I.A. should refer all enquiries regarding delivery of "A.R." direct to their Divisional Secretary and not to "A.R." direct. Non-members of the W.I.A. should write to the Victorian Division, C/o. P.O. Box 36, East Melbourne. Two months' notice is required before a change of mailing address can be effected. Readers should note that any change in the address of their transmitting station must be P.M.G. regulation, be notified to the P.M.G. in the State of residence; in addition, "A.R." should also be notified. A convenient form is provided in the "Call Book".



Direct subscription rate is \$3.50 a year, post paid in advance. Single copies 30c, issued monthly on first of the month. February edition excepted.

CONTENTS

Technical Articles:—

A Transverter for 21 or 28 Mc.	6
Project—Solid State Transceiver, Part Two	7
S.S.B. Transmitter—An Amateur Engineering Project, Part Three	11

W.I.A. Federal Executive:—

Federal Comment—The Year in Review	5
World Administrative Space Radio Communications Conference	16

General:—

Correspondence	19
DX	17
Index to Volume 36—1968	24
Overseas Magazine Review	14
Prediction Charts for December 1968	18
Publications Committee Report ..	16
Silent Keys	16
State Intruder Watch Co-ordinators	18
Tesla Equipment in Australia	16
VHF	18
W.I.A. D.X.C.C.	16

Contests:—

Contest Calendar	18
National Field Day	18
Ross Hull Memorial VHF/UHF Contest, 1968-69	10

W.I.A. OFFICIAL BROADCASTS

NEW SOUTH WALES

VK2W1, Sundays, at 1000 hours E.A.S.T.
3595 Kc. a.m. 145.130 Mc. a.m.
7148 Kc. a.m. 145.600 Mc. f.m.
53.865 Mc. a.m. 153.550 Mc. f.m.
proposed shortly)

VICTORIA

VK3W1, Sundays, at 1030 hours E.A.S.T.
1825 Kc. a.m. 144.500 Mc. a.m.
3600 Kc. s.s.b. 145.254 Mc. f.m.
7146 Kc. a.m. 432.500 Mc.
53.632 Mc. a.m.

QUEENSLAND

VK4W1, Sundays, at 0900 hours E.A.S.T.
3580 Kc. 53.995 Mc.
7148 Kc. 144.36 Mc.
14.342 Mc.

SOUTH AUSTRALIA

VK5W1, Sundays, at 0900 hours C.A.S.T.
3625, 7146, 14195 Kc. Also selected frequencies in 52 and 144 Mc. bands.

WESTERN AUSTRALIA

VK6W1, Sundays, at 0930 hours W.A.S.T.
3.655 Mc. s.s.b. 52.656 Mc. F3
7.080 Mc. a.m. 52.4 Mc. a.m.
14.100 Mc. s.s.b. 144.36 Mc. a.m.

TASMANIA

VK7W1, Sundays, at 1000 hours E.A.S.T.
3672 Kc., and re-transmitted by representative stations on—
7148 Kc. 144.1 Mc.
53.032 Mc. 432.6 Mc.

HY-GAIN (U.S.A.) ANTENNAS AND BEAMS

- 14AVQ 40 through 10 metres, and 18AVQ 80 through 10 metres Trap Verticals.
- 103BA, 153BA, 204BA Mono-band Beams for 10, 15 and 20 metres.
- TH6DXX, TH3MK3, TH3Jr Tri-band Beams.
- 2BDQ and 5BDQ Multi-band Trap Dipoles.
- 18TD Reel Tape Portable Dipole, 10 through 80 metres.
- C.I. Special Plastic Dipole, mil. spec., centre insulator, accepts 1/4" or 3/8" co-ax.
- E.I. Rugged 7" End Insulators for multi-band or single band dipoles.
- BN-86 all band H.F. Ferrite Baluns for Beams and Dipoles.
- Selection of spare parts for replacement purposes.

ALSO A LARGE RANGE OF V.H.F. ANTENNAS—

6 mx and 2 mx Ground Planes, V.H.F. Mobile Whips, 6 mx and 2 mx Halos. SJ2S4 4-element 2 mx stacked Vertical Jay-Pole. V.H.F. Beams, DB62 Duo-bander for 6 and 2 mx, LP62 Log Periodic for 6 and 2 mx, 215B 15-element 2 mx, 28B 8-element 2 mx, 23B 3-element 2 mx, 66B 6-element 6 mx.

Imported from U.S.A. by HY-GAIN ELECTRONIC PRODUCTS (AUST.) PTY. LTD.

Distributors: **BAIL ELECTRONIC SERVICES**

60 SHANNON STREET, BOX HILL NORTH, VIC., 3129

Phone 89-2213

Rep. for N.S.W.:—

A. J. BRUCESMITH

47 HYMAN ST., TAMWORTH, N.S.W., 2340

Phone (STD 067) 66-1010

GELOSO

SIX-BAND AMATEUR RECEIVER



Geloso

G4/216

AMATEUR PRICE:

\$225.60

plus Sales Tax 25%

Geloso Transmitters, VFO's and Receivers have been sold in Australia for 20 years, giving utmost satisfaction. Performance of a well designed and engineered Receiver is guaranteed by Geloso—ask a man who owns one. The G4/216 has everything modern about it. The front-end is xtal controlled. It has a crystal filter and crystal calibrator incorporated. Sensitivity, stability and selectivity are top notch for Amateur work. Finally, stocks are available from our warehouse. Send for bulletin number 103. It tells you all about the G4/216.

TECHNICAL DETAILS

Frequency Ranges: 10 metre band (28-30 Mc.), 15 metre band (21-21.5 Mc.), 20 metre band (14-14.5 Mc.), 40 metre band (7-7.5 Mc.), 80 metre band (3.5-4.0 Mc.); 144-146 Mc. (26-28 Mc.) for external VHF Converter.

Intermediate Frequency Rejection better than 70 db.

Sensitivity better than 1 μ V. for 1 watt a.f. output.

Signal-to-Noise Ratio at 1 μ V. better than 6 db.

Selectivity: Five positions—normal, xtal 1, xtal 2, xtal 3, xtal 4.

Reception of Amplitude Modulated Signals.

Reception of Single-Sideband Signals (s.s.b.): Amplifier and detector circuit for s.s.b. signals, with carrier re-insertion.

Noise Limiter: Effective with all types of signals. Self-adjusting to various signal levels.

SOLE

AGENTS:

R.H. Cunningham
PTY. LTD.


608 COLLINS STREET, MELBOURNE, VIC., 3000
Telephone 61-2464

64 ALFRED STREET, MILSONS POINT, N.S.W., 2061
Telephone 929-8066

radioparts

PROPRIETARY LIMITED

CUSTOMER SERVICE

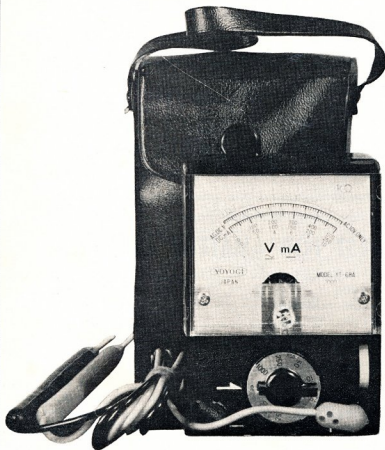

'RAPAR' MULTI-TESTER

MODEL YT 68A
MULTIMETER

Pocket Size: 2.4" x 3.3" x 1.2".

SPECIFICATIONS:

DC Voltage: 0 to 10, 50, 250, 1,000V.

AC Voltage: 0 to 10, 250, 500V.

DC Current: 0 to 250 mA.

Resistance: 0 to 100K.

Battery: 1.5V. (1 x 915).

Weight: about 7 oz.

A powerful magnet is mounted on the back of the case which enables the instrument to adhere to all steel surfaces.

The tester has a meter sensitivity of 1,000 O.P.V.

\$9.00 including tax



RADIO PARTS PTY. LTD.

MELBOURNE'S WHOLESALE HOUSE

562 Spencer St., Melbourne, Vic., 3000. Phone 329-7888, Orders 30-2224

City Depot: 157 Elizabeth Street, Melbourne, Vic., 3000. Phone 67-2699

Southern Depot: 1103 Dandenong Rd., East Malvern, Vic., 3145. Ph. 211-6921

OPEN SATURDAY MORNINGS!

SIDEBAND ELECTRONICS ENGINEERING

If you like to keep informed on the latest developments in our game and are also interested to hear what I have to say, just get on the mailing list for my monthly NEWS-SHEET.

For the Christmas shopping period there are special bargains and premiums on package deals. Here is my list of stocks:

GALAXY V. Mark III. Transceivers, using a pair of final tubes that were recently tested in Sydney under laboratory conditions, providing 380w. PEP output, the smallest powerhouse with the best receiver of the lot, \$550.

SWAN SW350C, SW500C, SW250 Transceivers, VOX units, combination AC/DC power supplies, literature and latest prices on request.

YAESU-MUSEN FLDX-400 Transmitters, FRDX-400 Receivers, FTDX-400 and FTDX-100 Transceivers, FLDX-2000 Linears, all cheaper than at any time before. Next year the latest addition, FT-200 Transceivers!

HY-GAIN TH6DX Master Triband Beams, with BN-86 balun, still only \$200.

HY-GAIN TH3JR Junior Beam, \$105. **MOSLEY TA33JR Junior Beam** \$98. Next year the senior brother of the Mosley Junior, the MP-33, target price \$125.

HAM-M CDR Heavy Duty Antenna Rotator, with indicator control unit 230v., \$180. **CDR AR-22 Rotator** for junior beams, also with control unit 230v., \$60.

NEWTRONICS Hustler 4-BTV 10-40 M Vertical, \$55. With 80 M top-loading coil, \$65.

GONSET Two Metre SSB/AM/CW Sidewinder Transceiver, \$350, including 115v. clip-on power supply.

MOBILE SUPPLIES, 12v. DC, extra heavy duty design with four 35A transistors, tested at half a kilowatt output, \$105.

WEBSTER Bandspanners, all-band centre-loaded Mobile Whips, with swivel mounting and spring, \$55.

MARK 10-15-20 M triband Helical Whip, \$27.50. **MARK 40 M Helical Whip**, \$16. German W3DZZ all-band Dipole, 110 ft. inverted vee span, balun with traps, \$25.

Spare valves for all Transceivers, **CETRON 572B/160TL**, 150w. Triodes, \$18.

TRIO TS-500 Transceiver with PS-500 speaker-supply, spotless demonstration units, \$450.

GELSO 209R Receiver, with speaker, good condition, \$125.

A large stock of brand new **NATIONAL** receiver power transformers and chokes, dozens of types, small and large, at give-away prices of from \$1 to \$2.50 each, pool orders to save on freight, ask for list. Arie Bles.

SIDEBAND ELECTRONICS ENGINEERING

P.O. BOX 23, SPRINGWOOD, N.S.W., 2777

Telephone: Springwood 511-394

BOOKS OF INTEREST FOR AMATEUR OPERATORS

★ A.R.R.L.—THE RADIO AMATEUR'S HANDBOOK—45th Ed., 1968 Edition	Price \$6.15 posted
★ A.R.R.L.—THE A.R.R.L. ANTENNA BOOK	Price \$3.05 posted
★ A.R.R.L.—HOW TO BECOME A RADIO AMATEUR	Price \$1.55 posted
★ A.R.R.L.—A COURSE IN RADIO FUNDAMENTALS	Price \$1.55 posted
★ A.R.R.L.—THE RADIO AMATEUR'S LICENSE MANUAL	Price \$0.90 posted
★ A.R.R.L.—THE RADIO AMATEUR'S V.H.F. MANUAL ..	Price \$3.85 posted
★ A.R.R.L.—SINGLE SIDEBAND FOR THE RADIO AMATEUR	Price \$3.75 posted
★ A.R.R.L.—UNDERSTANDING AMATEUR RADIO	Price \$3.15 posted
★ STONER & EARNSHAW—THE TRANSISTOR RADIO HANDBOOK	Price \$6.75 posted
★ MIVEC—RADAR, PRINCIPLES AND PRACTICES	Price \$5.30 posted
★ ELECTRONICS AUSTRALIA—BASIC RADIO COURSE	Price \$1.65 posted
★ ORR—MOBILE HANDBOOK	Price \$3.45 posted
★ DOUGLAS & ASTLEY—TRANSISTOR ELEC. ORGANS FOR THE AMATEUR ..	Price \$3.15 posted
★ HANDEL—A DICTIONARY OF ELECTRONICS	Price \$1.40 posted
★ ORR—RADIO HANDBOOK, 17th Edition	Price \$13.60 posted

McGILL'S AUTHORISED NEWSAGENCY

Established 1860

The G.P.O. is opposite

183-185 ELIZABETH STREET, MELBOURNE, VIC., 3000

Phones 60-1475-6-7

FEDERAL COMMENT

The Year in Review

As mentioned in last month's issue, the development of Region III. activities has probably been the highlight of the year. Since the Federal President's comment we have now received agreement to the Region III interim constitution from the Philippines. In a letter from Emilio DUIEA, a further amendment is made to the status of the Amateur Radio organisation in that country, and we can do no better than quote the relevant section:

"In view of the establishment of a new organisation of Radio Amateurs in the Philippines, viz. 'Philippine Amateur Radio Service Inc.' (P.A.R.S.), the other Societies—P.A.R.A. and P.A.R.L.—are now only chapters of P.A.R.S. The P.A.R.S. will now replace P.A.R.A. for purposes of membership with the I.A.R.U., and is the only organisation, of which I am the President, recognised by the Philippine Government".

We congratulate Emilio and note with interest his last point.

Our domestic scene can be viewed in the light of progress, too, and arising from the Federal Convention discussions last Easter, a committee was formed to investigate all aspects of "A.R." By the time this is read, copies of the report should be in all Divisions and you are urged to read it and become informed of the many problems confronting the Editor and his Committee.

Nearly all matters arising from this Convention have been dealt with, although a proposal that some sort of code proficiency test be run is still being worked out in conjunction with the VK7 Division.

We also saw the very liberal provisions by the Postmaster-General's Department in reply to our request to use v.h.f. repeaters, and in the subsequent enthusiasm resulting in a conference at Wodonga, many plans have been made for operational repeaters. This Institute felt that the frequencies and modes proposed were worthy of adoption as policy and they are being considered by Divisions. There does appear, however, to be some aspects at variance with the Tasmanian group's thoughts on the matter and it is hoped that the VK2 repeater secretariat can assist in providing a solution.

Whilst speaking of v.h.f., we would refer you to the published statement, shown elsewhere in this issue, from the I.T.U. Administrative Council. Any comment from us at this stage would be pure speculation, but you should be aware that we are being kept informed of all and any developments. When a more specific agenda is available—perhaps during the middle of this coming year—we will know a little more, and can form a more specific judgment. Whilst our Amateur bands 144 Mc. and above are slotted into the part of the spectrum under review, the preparations to try and counter any inroads by other services are no less stringent than they would be for h.f. bands.

Your Federal Councillor and Division will be asking you for reports on v.h.f. activities and achievements, and we suggest that this information be provided as soon as possible. The significance of this information, or the lack of it, will be obvious.

It is interesting to note that in this country, the number of civil radio

communication stations between 148 and 174 Mc. amounted to 14,500 over twelve months ago. In nine months, the total number of stations in Australia increased from 93,000 to 102,000—so the commercial and civil users have their problems too.

Before leaving you with thoughts of holidays and/or the work to be done around the house, we should mention that you could find time perhaps to suggest ways of improving the national society that represents you, viz. the W.I.A., or the conditions under which we are allowed to operate.


Next Easter, the Federal Convention may be held in Canberra, but no matter where, all Federal Councillors will meet to consider and review past policies, up-date them if necessary, and introduce new ones.

Your suggestions are valued and your Division will be eager to consider all proposals put before it, no matter if it concerns DX, contests, regulations, finance or administration—so while dangle that line or contemplating the beauty of your favourite holiday retreat, why not slip in the thought to do something positive when you return to civilisation?

In the meantime, our best wishes for a pleasant and relaxing Christmas season, with a prosperous 1969 in the offing. With 73 from Federal Councillors: Pierce VK2APQ, Deanne VK-3TX, David VK4DP, Geoff VK3TY, Neil VK6ZDK, Ted VK7EJ, and your Federal Executive: John VK3OR, Michael VK3KL, Peter VK3IZ, David VK-3QV, George VK3VX, Alf VK3IE, and Kevin VK3ARD.

AL RECKNER.* VK5EK

(Continued on Page 15)

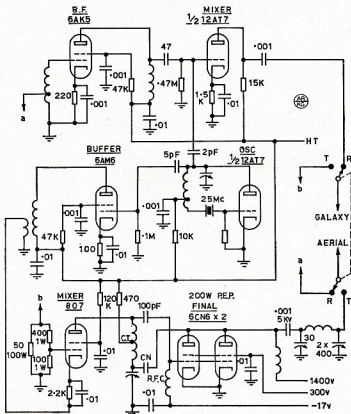

A TRANSVERTER FOR 21 OR 28 Mc/s

PROJECT—SOLID STATE TRANSCEIVER

PART TWO

H. L. HEPBURN,* VK3AFQ, and K. C. NISBET,† VK3AKK

In this second part of the series of articles on a modularised transceiver, it is proposed to deal with the receiver "front-end" and the injection oscillator chain which is common to both receiver and transmitter.

RECEIVER FRONT-END

Reference to Fig. 1 in the November 1968 issue of "A.R." (included here for convenience of readers) shows that the front end of the receiver consists of Function 1 (receiver r.f. amplifier) and Function 2 (receiver mixer).

Fig. 5 in this article gives the circuit diagram for these functions, while Table 2 lists coil data for the usual h.f. Amateur bands.

Before proceeding with a detailed description of the circuit a general comment must be made.

One of the biggest problems involved in the design of multiband equipment, no matter whether receiver, transmitter or transceiver, is not an electrical one. In the authors' view the problem is mechanical—the physical layout of components associated with the conventional multi-wafer band switch. If, say, a four-band device is required, it is necessary right at the start of building to make provision for the correct number of switch wafers, coil forms, etc., to be in the right position to give minimum lead length. In all probability too, it is necessary to fit metal screens between the various sections. If, later, you want to add a band you are stuck with the original layout and metalwork and can only achieve your objective by recourse to extensive surgery.

In attempting—as this series of articles does—to present a completely flexible design—the need rigidly to fix the physical layout beforehand could not be tolerated. To a very large degree the problem has been overcome by eliminating the need for a complex switch.

The band switch for the whole receiver has been reduced to a single bank selecting the appropriate antenna coil coupling link (L1, Fig. 5) and the 10v. feed rail to each front-end board. This switch bank is physically removed from the boards and connected thereto by co-ax. The outputs of all boards are connected in parallel and are not switched at all.

To eliminate completely any slight puzzlement that may have been caused by reference to front-end boards in the plural, let it be emphasised that there is one complete set of semiconductors and coils for each band covered.

Whilst it is admitted that the approach used is slightly more expensive than the conventional one, it is the only one, in the writers' view, that could be used if the completely flexible modular principle was to be upheld.

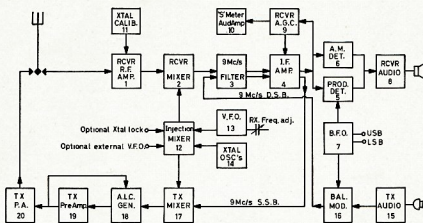


FIG. 1—TRANSISTOR-4 BAND-TRANSCEIVER—BLOCK DIAGRAM.

	L1 Input	L2, 3, 4, 5 RF/Mixer Tuned	L7, L8 Oscillator Input	C1, C2 C3, C4	C5, C6	C7	R* RF Source
Band	Link	Circuits	Filters	pF.	pF.	pF.	Resistor
160	10t, 39g.	80t, 39g.	38t, 28g.	470	47	470	Nil
80	10t, 39g.	50t, 39g.	30t, 28g.	150	47	470	Nil
40	7t, 28g.	34t, 28g.	25t, 28g.	150	47	470	Nil
20	7t, 28g.	34t, 28g.	34t, 28g.	33	100	1000	Nil
15	5t, 28g.	20t, 28g.	20t, 28g.	33	47	470	10.0K
10	5t, 24g.	16t, 24g.	25t, 28g.	33	22	220	3.9K

TABLE 2—RECEIVER FRONT-END COIL DATA

Notes on Table 2 and Figure 5:—

1. L6 is 38 turns of 28 gauge B. & S.
2. All coils close wound on Neosid Type 722/1 bakelite coil formers.
3. All coils use Neosid F29 tuning slugs.
4. L2/3, L4/5, and L7/8 are mounted 15/32 inch apart to form band pass coupled pairs.
5. L1, the antenna coupling link is close wound over the earthy end of L2.
6. All coils are wound with specified gauge of B. & S.

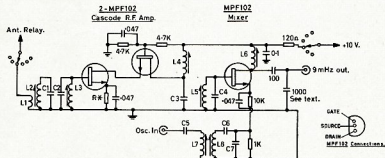


FIG. 5—4 BAND TRANSISTOR TRANSCEIVER—RX FRONT END.

* 4 Elizabeth Street, East Brighton, Vic., 3187.
† 25 Thames Avenue, Springvale, Vic., 3171.

Each front-end printed circuit board is "wired" for two bands so that the four bander as designed uses two p.c.b.s. It is possible to extend the coverage of the unit up to eight bands if desired simply by adding further boards. No mechanical alterations are needed.

The circuitry for each band is shown in Fig. 5.

A fixed tuned, mutually coupled, pair of coils (L2/L3) feeds the gate of the "bottom" half of a cascode r.f. amplifier using Motorola MPF102 single gate FETs. The source resistor marked * on the diagram has the primary purpose of keeping the gain constant from band to band. For 160/80/40/20 metres, it is not needed at all.

The gate of the "top" half of the cascode is maintained at half rail potential by the two 4.7K resistors and earthed for r.f. by the 0.047 μ F. capacitor.

The r.f. drain coil (L4) is mutually coupled to the mixer gate coil (L5) and proper adjustment of these and the r.f. amplifier coils enables the correct band pass to be achieved.

C5/L7 forms a series tuned circuit on the required injection frequency which is mutually coupled to L8. This latter coil is parallel tuned by the combination of C6 and C7 in series. The low impedance output required by the source method of injection into the mixer is obtained from the junction of C6 and C7.

The reason for the inclusion of L7/L8 is to ensure a pure injection waveform. This is covered more thoroughly in the section following.

The mixer proper is a third MPF102 with a 9 Mc. tuned circuit in the drain. This coil (L6) is tuned by the series combination of the 100 pF. and 1,000 pF. capacitors. Output at low impedance is taken from the junction of the two capacitors. Note that the 1,000 pF. is only needed on the first board made.

Since all board outputs are in parallel, this single 1,000 pF. will effectively be in series with the 100 pF. capacitors on the individual boards. It is of course necessary to re-peak the various L6s when adding more bands because there is some slight interaction between them.

A.g.c. is applied by varying the d.c. applied to the h.t. rail. The method of deriving a supply voltage which varies inversely with signal will be discussed in a later article. Provision is also made for a manual r.f. gain control by the same method of varying the h.t. rail.

INJECTION OSCILLATOR CHAIN

The three component parts of the oscillator chain are the functions marked 12, 13 and 14 in Fig. 1. They are detailed in this article in Figs. 6, 7 and 8 with the coil data being given by Tables 3, 4 and 5 respectively.

In general, the higher the operating frequency of the v.f.o., the simpler it is to prevent spurious responses. However, there are some obvious difficulties in constructing a really stable v.f.o. at frequencies in the 40-50 Mc. region and, after considerable experiment, the method adopted has been to operate the v.f.o. on 10-10.5 Mc., heterodyne this with a fixed crystal oscillator to

56-56.5 Mc. and then heterodyne down to the required injection frequency with a series of high frequency crystal oscillators.

With a fixed i.f. of 9 Mc. the injection frequencies needed for the various Amateur bands (and the heterodyne crystal frequencies needed to come down from 56-56.5 Mc.) are given in Table 6. Note that in all cases the b.f.o. operates on the u.s.b. crystal and that the correct sideband for the band in use is automatically selected if the specified heterodyne crystals are used. The "other" sideband is available by using the l.s.b. crystal in the b.f.o.

Note, too, that since the same injection frequency is used for both transmit and receive, there can be no offset. If the receiver is tuned to a signal on any band the transmitter comes up on exactly the same frequency and sideband. In many cases, such as participation in round tables, this may be a disadvantage and provision is made for

a received frequency offset facility. This will be described later in the series.

The apparent complexity of the injection train needs comment. However, closer scrutiny will show that there are only a couple of additional stages over the complement of stages normally found in a transceiver. The v.f.o. and crystal heterodyning stages and their associated mixers are common to all current designs. The one vital addition is the 46 Mc. oscillator and its mixer in the v.f.o. generator. This takes the virtual output of the v.f.o. up to 56-56.5 Mc. The reason for this can be summed up in one word . . . "birdies".

Rather than plough through the mathematics involved, a description of a practical test may be simpler.

The writers carried out a series of tests on four popular commercial sideband rigs and one very good "home brew" job. The test was simple and was as follows:

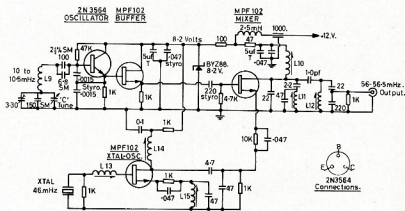


FIG. 8-4 BAND TRANSISTOR TRANSCEIVER - VFO GENERATOR.

Coil	Freq. Mc.	Turns	Wire Gauge B. & S.
L9	10-10.5	22	20 approx.
L10	56-56.5	12	20
L11	46 (trap)	12	20
L12	56-56.5	12	20
L13	—	10	28
L14	46	20	28
L15	30-32 approx.	15	28

TABLE 3.—VFO GENERATOR COIL DATA

Notes on Table 3 and Figure 6:—

- All coils close wound on Neosid Type 722/1 bakelite formers.
- L9 is $\frac{3}{8}$ " diameter, 16 turns per inch, "Willis" air wound inductance No. 3-16 (or B. & W. No. 3011), obtainable from William Willis and Co. Pty. Ltd., 430 Elizabeth St., Melbourne.
- The tuning condenser C_{TOSSE} is an Edystone No. 585 4.5 to 91 pF. single section variable.

The receiver under test was set to 14.2 Mc. and a signal of 10 mV. fed to the antenna terminal. Note that 10 mV. is (roughly) equal to a "S9 + 40 db." signal. The equivalence may not be exact, but is quoted to indicate that 10 mV. is a large, but not unlikely, signal.

The signal generator was then swept over the range 8-25 Mc. (keeping the 10 mV. input constant) and the number of audible beats counted. There is nothing magical about the range chosen—it just happened to be the range with 14 Mc. approximately in the middle.

On all the units tested there were between 10 and 18 spurious responses in the receiver of strengths varying between less than S1 up to S6.

Each one of these spots represented a frequency, which, if occupied by a powerful signal, would give an unwanted "stranger" in the 14 Mc. Amateur band. (Are you absolutely certain that strong teletype signal really is on 20 metres?)

In general the possibility of spots can be traced to the use of low frequency heterodyning techniques and the difficulty, at lower frequencies, of removing harmonics from the injection chain.

Page 9

ROSS HULL MEMORIAL VHF/UHF CONTEST, 1968-9

The Federal Contest Committee of the Wireless Institute of Australia invites all Australian and Overseas Amateurs and Short Wave Listeners to participate in this annual Contest which is held to perpetuate the memory of Ross Hull whose interest in v.h.f./u.h.f. did much to advance the art.

A Perpetual Trophy is awarded annually for competition between members of the W.I.A. in Australia and its Territories, inscribed with the name and life work of the man whom it honours. The name of the winning member of the W.I.A. each year is also inscribed on the Trophy. In addition, this member will receive a suitably inscribed certificate.

OBJECTS

Australian Amateurs will endeavour to contact as many other Amateurs in Australia and Overseas under the following conditions.

DATE OF CONTEST

From 0001 hours E.A.S.T., 7th December, 1968, to 2359 hours E.A.S.T., 12th January, 1969.

DURATION

Any seven calendar days within the dates mentioned above, not necessarily consecutive. These periods are to be at the operator's convenience. A calendar day is from 0001 hours E.A.T. to 2359 hours E.A.T.

RULES

1. There are two divisions, one of 48 hours duration, and one for seven days. In the seven-day division, there are three sections:

- (a) Transmitting, Open.
- (b) Transmitting, Phone.
- (c) Receiving, Open.

2. All Australian and Overseas Amateurs may enter for the Contest whether their stations are fixed, portable or mobile.

3. All Amateur v.h.f./u.h.f. bands may be used, but no cross-band operation is permitted. Operators are cautioned against operating transmitting equipment on more than one frequency at a time, particularly when passing cyphers. Cross-band operation to assist contest working is prohibited.

Such operation will be grounds for disqualification. Cross mode contacts will be permitted.

4. Amateurs may enter for any of the transmitting sections. The seven-day winner is not eligible for the 48-hour award.

5. Only one contact per band per station is allowed each calendar day.

6. Only one licensed Amateur is permitted to operate any one station under the owner's call sign. Should two or more operate any particular station, each will be considered a contestant and must submit a separate log under his own call sign.

7. Entrants must operate within the terms of their licences.

8. **Cyphers:** Before points may be claimed for a contact, serial numbers must be exchanged. The serial numbers of five or six figures will be made up of the RS (telephony) or RST (c.w.) report plus three figures, commencing in the range 001 to 999, for the first contact, and will then increase in value by one for each successive contact. When a contestant reaches 999 he will then commence again with 001.

9. **Entries must be set out as shown in the example, using only one side of the paper. Entries must be post-marked not later than 10th February, 1969, and clearly marked "Ross Hull Contest" and addressed to Federal Contest Manager, Box N1002, G.P.O., Perth, W.A., 6001.**

10. **Scoring for all sections will be based on the attached table. Distances must be shown in the log entry as shown in the example. Failure to make this entry will invalidate the particular claim. Some typical distances are given in the attached table.**

11. **Logs:** All logs shall be set out as in the example and in addition will carry a summary sheet showing the following information:

Name.....Call Sign.....
Address.....Division.....
.....Claimed Score.....

SCORING TABLE

Distance in Miles	52 Mc.	144 Mc.	432 Mc.	576 Mc.	Higher
Up to 25 Miles	1	1	2	2	20
26 to 50 "	1	1	10	10	50
51 to 100 "	2	5	25	30	100
101 to 200 "	5	10	50	60	200
201 to 300 "	15	15	75	85	250
301 to 500 "	10	20	100	125	300
501 to 1050 "	5	25	200	200	350
1051 to 1500 "	10	50	250	250	400
1501 to 2500 "	20	100	300	300	450
2501 to 3500 "	35	200	400	400	500
3501 to 5000 "	50	300	450	450	550
5001 and over	100	400	500	500	600

Operating Dates.....(7 cal. days)
Highest Score over a 48-hour period was.....points.

Operating period:
from.....hrs. E.A.T. /...../6...
to.....hrs. E.A.T. /...../6...

Declaration: I hereby certify that I have operated in accordance with the conditions of my licence and abided by the Rules of the Contest.

Signed.....
Date.....

12. Entrants not abiding by the Rules of this Contest will be disqualified.

13. The ruling of the Federal Contest Committee of the W.I.A. will be final. No dispute will be entered into.

14. **Awards:** Certificates will be awarded to the winners of each section in each VK and Overseas Call Area. The VK contestant who returns the highest score in the transmitting section and who is a financial member of the W.I.A., will have his name inscribed on the Trophy which will be held by his Division for the prescribed period. A Certificate will be awarded to the contestant who shall not be the Trophy winner, and who returns the highest scoring log covering a period of any 48 consecutive hours.

Also, Certificates will be awarded for operating in the Ross Hull Contest and breaking any Australian v.h.f./u.h.f. distance record.

RECEIVING SECTION

1. Short Wave Listeners in Australia and Overseas may enter for the Contest, but no transmitting station may enter.

2. Contest times and logging of stations on each band are as for the transmitting sections, however there is no 48 hour sub-section.

3. To count for points, logs will take the same form as for transmitting sections, but will omit the serial number received. Logs must show the call sign of the station heard (not the station worked), the serial number sent by it, and the call sign of the station being worked.

Scoring will be on the same basis as for transmitting stations, i.e. on the distance between the Listener's station and the station heard. See the examples given. It is not sufficient to log a station calling CQ.

4. A station heard may be logged only once per calendar day on each band for scoring purposes.

5. **Awards:** Certificates will be awarded to the highest scorer in VK and Overseas countries.

EXAMPLE OF TRANSMITTING LOG (Brisbane Station)

Date/Time E.A.S.T.	Band Mc.	Emission	Call Sign	RST/No. Sent	RST/No. Rcvd.	Dist. Miles	Points Claimed.
24th Dec. 0100 E.A.S.T.	52	A3(a)	VK7ZAI	59001	59004	1110	10
0110 E.A.S.T.	52	A3(a)	VK4NG	58002	57051	330	10
0230 E.A.S.T.	144	A3	VK5ZK	59003	55043	990	25
0235 E.A.S.T.	144	A3	VK3ZJO	45004	46021	850	25

EXAMPLE OF RECEIVING LOG (Perth S.w.I.)

Date/Time E.A.S.T.	Band Mc.	Call Heard	RST/No. Sent	Station Called	Dist. Miles	Points Claimed
2nd Jan. 0000 E.A.S.T.	52	VK5ZDX	59221	VK8KK	1330	10
1025 E.A.S.T.	52	VK2ZCF	58195	VK6ZAA	2040	20
1110 E.A.S.T.	432	VK6ZDS/6	57061	VK6LKL/6	60	25
3rd Jan. 0000 E.A.S.T.	144	VK5ZHU	44102	VK5ZCN	1330	30

S.S.B. Transmitter—An Amateur Engineering Project

PART THREE

H. F. RUCKERT,* VK2AOU

SECOND MIXER AND CRYSTAL OSCILLATOR

The second mixer is basically identical to the first one. One can use a balanced mixer with a twin triode, and different valves and a variety of operating conditions were tried, or a mixer valve like the 6AJ8, etc., with screen grid shielding to prevent the oscillator signal appearing at the plate may be tried as the writer did.

The following problem occurred: The linear p.a. was on a separate chassis and no tuned grid circuit was provided. The driver tank employed caused, on 10 metres, a substantial downward drive voltage transformation, due to the ratio of driver plate capacity to p.a. grid capacity. Changing the L-C ratio at the driver plate circuit did not help much due to mismatch.

The 12BY7 driver used at the time was already working in class AB1 and could not take a higher grid input voltage (or grid current would occur, causing flat-topping) to obtain more drive on 10 metres. The gain, using a 6BA6 pre-amplifier with wide band damped tuned circuits, was only about 4, and the second mixer 6AJ8 gain was 1.5 to 2 with a similar tuned circuit. This mixer could not be driven harder without causing distortion here or in the first mixer. A further difficulty was encountered due to the crystal oscillator being remote in the nearby standing receiver, operating at the 1-2 volt level required for the receiver 6U8 mixer valve. Less than 1 v. r.f. was left at the end of 18 inches of co-axial cable at the transmitter second mixer.

The mixer input signal should be no higher than 10% of the oscillator voltage, which means that under these conditions the placement of stages made it impossible to obtain sufficient drive for 15 metres and the two 10 metre ranges. At this stage one can either scrap the design, pull everything out, pieces and start with a new chassis again—if one feels like it—or solutions have to be found which can easily be incorporated. There was no space for additional valves and tuned circuits with band switches.

It was found that a ferrite balun transformer with 4 x 8 turns (the type used as t.v. $\frac{1}{2}$ " x $\frac{1}{2}$ " aerial balun) gave a voltage gain of 4 over the required range from 8 to 33 Mc. and matched the 300 ohm co-axial cable between receiver and transmitter mixer. This balun was a most efficient wide band amplifier.

The second mixer was slightly modified to suit the available 8-10v. oscillator voltage, making it possible to use 1v. s.s.b. input signal. The output of 2v. s.s.b. signal was twice that delivered by the 6AJ8 mixer. It would have been a great help if the published equipment descriptions had shown the d.c. and r.f. voltages and d.c. currents.

The crystal oscillator circuit is usually used with overtone crystals like those

here employed for the 15 and 10 metre operation (25.45, 32.45 and 32.95 Mc.), but works just as well on the fundamental frequency of the other crystals. Band switching is so very much easier than with the circuit recommended by the crystal manufacturer. A 6AM6 triode connected is employed in the oscillator. A 6AK5 pentode connected buffer stage is used, which gave more output than a cathode follower which was also tried. This was a matching problem. The grids of cathode followers must not be driven into grid current, as sometimes insufficient voltage is obtained also due to unity gain of these stages. Next time the c.o. will be placed close to the second mixer.

Trying to use surplus crystals which were etched or lapped to the frequencies required was only a disappointing experience. With these the receiver had many more spurious beat notes than those precalculated, and the output was too low on overtones or harmonics. The new locally manufactured crystals were excellent in every respect. They were the only expensive item the writer had to buy to build this transmitter. The 10 pF. and 7 pF. series capacitors pull these crystals to the required frequency.

PRE-AMPLIFIER AND DRIVER

To be able to step up the drive power the 6BA6 pre-amplifier was replaced by a 12BY7, and the 12BY7 driver was replaced by a 6BQ5 pentode. These valves with their higher plate current operating in class AB1 match better the damped wideband tuned circuits. Plenty of clean drive is now available on all bands.

Using valves with relatively high grid 1 to plate capacity may call for neutralising. In this case, good shielding between stages, a small earthed plate between grid and plate valve pins, stray field preventing Q ferrite slugs in the coils (not in driver plate coils), grid stopper resistors, ferrite stopper rings at grid 1 and plate of the driver, the driver loading by the final space charge capacity effect, and the anyhow necessary damping resistors parallel to tuned circuits kept things under control without neutralisation.

With the different L-C ratio of the tuned circuit and damping resistors, these two stages are able to deliver uniform drive power at 55v. r.m.s. to the final at all operating frequencies between 3.5 and 29.0 Mc. Minor deficiencies can be compensated with the drive control (5K ohm) in the cathode of the 12BY7 (ratio 1:3 at the most).

The pre-amplifier tuned circuits are tuned to a frequency 10% higher than the lower band edge, and the second mixer plate tuned circuits are set to a frequency 10% below the upper band edge. Under these conditions the 12BY7 has a gain of up to six and the 6BQ5 achieves a gain of six at 10 metres and 20 at 80 metres after pi filter transformation (measured at the grid

of the final) with the driver plate circuit tuned to the exact working frequency.

LINEAR POWER AMPLIFIER

This transmitter occupies a quarter of the volume the a.m. rig it replaces, and the weight is also down to 30%. On the other hand, there were no plans to build a minibox without leaving air space inside to fit in the glove box of the car. It should be possible to run the final at full legal power all day and not just for 30 seconds as recommended by some transceiver manufacturers (tune-up condition) to prevent the glass of the final valves from softening. Using a 200w. capability exciter followed by a 400w. linear does not appear very economical either. The final valves were to be operated close to the manufacturer's class AB1 specifications.

There were still the 25 years old but very modern looking all glass Teufelchen radar valves, Type LS50, in my collection. Their size is similar to a 6146 but plate dissipation is 40w., which is ideal for the experiments intended to carry out. Their plate current was only half that of the 6146, but by using three valves in parallel with slightly higher screen and plate voltage the legal power max. of 400w. p.e.p. output with double tone input and zero grid current could be obtained with 55v. r.m.s. as drive potential.

The total valve capacities were similar to 1 or 2 more modern valves:

For three valves in parallel—
Input C: 45 pF.
Output C: 30 pF.
Grid-Plate C: <0.27 pF.
gm: 12 mA/V.

The valves require little filament power, being 12.6v. x 3 x 0.75a.

There is not much wrong with certain older valves, and I am grateful to DLIFK for a few more valves of the same type.

Also the three valve holders of the linear p.a. are mounted above the chassis. Their connecting pins (except grid 1 and plate) are soldered to tubular 1,000 pF. feed-through capacitors. 0.01 μ F. disc (marked) capacitor are soldered parallel to the 1,000 pF. capacitors—just in case. A shielding strip runs across the valve holder and through a slot between grid 1 and plate pin. $\frac{1}{2}$ " wide sheet copper strips have been used to wire r.f. carrying components.

At first no v.h.f. plate suppressors were used when the transmitter worked only on 80, 40 and 20 metres. Some instability was observed on 15 metres, and something had to be done before 10 metres could be used. The usual 50 and 100 ohm resistors with a few turns of wire wound around the resistor as a choke were working fine on 20 and 15 metres, but on 10 metres these resistors went up in smoke. It was found that more than two turns caused such

Amateur Radio, December, 1968

and the other trimmer is set to obtain zero reading. The resistance of the meter movement including shunts and dropping resistors represent the diode load and determine the diode characteristic and s.w.r. reading obtained. This meter was an r.f. amp. meter with burnt out thermo-cross. The meter scale figures are, at low s.w.r. levels, nearly the right s.w.r. values, as a calibration with various load resistors showed.

Forward reading four divisions, 52 ohms, 1:1 s.w.r.

Reverse Reading (Original Marking)	S.W.R.
1.6	1.5
2.25	2
2.5	2.5
2.75	3
2.9	3.5
3.15	4
3.3	5

The two Gc diodes should be matched. This s.w.r. and r.f. watt meter serves also as p.a. tuning indicator.

POWER SUPPLIES

Heavy filter chokes, large paper capacitors and the 866 rectifiers are now obsolete. The silicon diodes and high capacity electrolytic capacitors take their place.

Exciter and final p.a. have their own power supplies built in, providing also regulated negative bias and regulated lower B+ voltages. The mains switches S15 (a, b, c) and S16 (a, b, c) have four positions:

- (1) Off.
- (2) Filaments and negative bias on.
- (3) H.t. and lower B+ on, via 1K ohm resistor to limit voltage and current peaks and to slow down the charging of the electrolytics.
- (4) Shortening the 1K ohm resistor to reduce circuit resistance to improve h.t. regulation.

To be able to use the available 2 x 350v. transformer for the exciter supply without obtaining a too high B+ voltage, not to make dropping resistors necessary which cause extra heat, small charging electrolytics were only used. These 2 x 4 μ F. capacitors must be able to stand up to the so-caused high ripple voltage and current without exploding.

The 220v./2 x 800v. h.t. transformer has been re-impregnated after its first



20 years of service which stopped some strange noises. With 240v. input, 2 x 940v. output are obtained. No filter choke, only a string of four 260 μ F. (200 μ F. nominal) electrolytic capacitors are used here. It may be vital to remember that the aluminium can is usually not insulated from the electrodes of the unit, no matter whether the positive and negative terminals are both available at the insulated base plate. Insulating sleeves are placed between can and clamp. Shunk-on plastic sleeves some capacitors have may not be sufficiently safe, they can crack if the components become too hot. A red neon pilot light indicated the charge of the electrolytic capacitors.

The bleeding action of the resistor chains, VR tubes and the screen current drain is quite rapid. Two screen grid voltages are available with the switch S5 from two multi-section neon stabilisers. A 30 μ F. electrolytic capacitor provides the extra screen grid power for occasional loud voice and drive

peaks, without having to use larger stabilisers capable of holding the voltage at >10 mA. screen grid current per p.a. valve. The h.t. voltage fluctuates with speech (s.s.b. modulation) by not more than $\pm 3\%$. The transmitter power is limited by the allowable heating up of the h.t. transformer, the screen grid current the 1S50 valves can take, and the regulation limitations of the U₁ stabilisers.

A convenient source for the -80 volt bias and 100 volt/40 mA. for the antenna relay was found at the centre tap of the primary winding of the h.t. transformer. A separate 200 mA. fuse was used. At one stage an electrolytic capacitor had lost its capacity, and did not therefore act as a charging capacitor any more, and so the stabiliser for the bias voltage did not fire, causing high bias voltage of the wrong value and ripple. Strong carrier and distorted audio was reported. The large capacitors now used leave only a few mV. ripple voltage.

(To be continued)

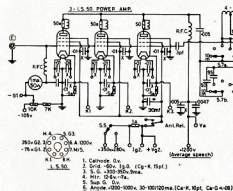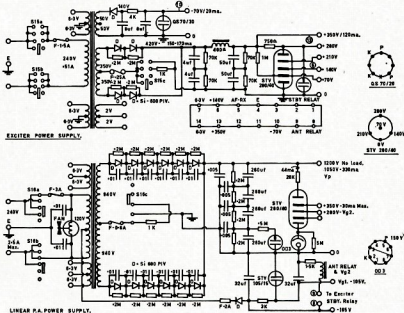

Solid State Transceiver

(Continued from Page 9)

Overseas Magazine Review

Band	Signal Mc.	Injection Mc.	S.B. Generated	Hetro. Xtal Mc.
160	1.8-2.3	10.8-11.3	LSB	45.20
80	3.5-4.0	12.5-13.0	LSB	43.50
40	7.0-7.5	16.0-16.5	LSB	40.00
20	14.0-14.5	5.0-5.5	USB	51.00
15	21.0-21.5	12.0-12.5	USB	44.00
10A	28.0-28.5	19.0-19.5	USB	37.00
10B	28.5-29.0	19.5-20.0	USB	36.50
10C	29.0-29.5	20.0-20.5	USB	36.00
10D	29.5-30.0	20.5-21.0	USB	35.50

TABLE 6.—FREQUENCY DATA

Notes on Table 6:—

1. In all cases the 9 Mc. sideband is generated on USB. On 160/80/40 this 9 Mc. USB is subtracted from the injection frequency to give LSB. On all other frequencies it is added to the injection frequency to give USB.

AVAILABILITY

As indicated in the previous article, kits and/or board and/or instructions will be made available at the following prices:

- (1) VFO generator complete with crystal and die cast box, \$35.25 each.
- (2) Injection mixer complete with die cast box, \$19.75 each.
- (3) Hetrodyne oscillators—
 - (a) 1st board, including board, die cast box and crystal, \$16.50 each.
 - (b) 2nd, 3rd and 4th boards, components and crystals, \$9.50 each.
- (4) Receiver front-ends—
 - (a) 1st and 3rd bands, including boards, \$9.75 each.
 - (b) 2nd and 4th bands, components only, \$7.75 each.

Postage on items 1, 2, 2a is 20c; on items 3b, 4a and 4b is 13c. Please address enquiries to 4 Elzabeth Street, East Brighton, Vic., 3187.

ERRATUM

Would readers please note an error in the circuit diagram of the receiver audio section (Fig. 2, Nov. 1968 "A.R."). A connection is shown between the collector of the AY1121 driver transistor and the 12-20 volt h.t. line.

This connection should not exist and the AY1121 collector is connected only to the base of the AY1120 device.



FORMER EDDYSTONE CHIEF HERE

Mr. Arthur Edwards (G6XJ), formerly managing director of Eddystone Radio (Stratton & Co. Ltd., Birmingham, U.K.), arrived in Melbourne on 4th December. An active Amateur, Mr. Edwards will stay in Australia for an indefinite period and will be operating call sign VK3AMM portable.

"RADIO ZS"

June 1968—

A De Luxe Mobile Power Supply: L. Uys and D. Brook. Using 2N2055s (four) to produce 650 volts at 100 mA. from 12v. battery. Efficiency about 80 per cent.

Do It With Diodes: C. de Souza. Discussion on using diodes to protect a number of electronic circuits.

July 1968—

The Ferrite Balun: J. Hugo, ZS1SC. Describes a method of making a balun using straight ferrite rod 40 cm. long. Balun can be made about three inches long should be suitable. 1/1 and 4/1 baluns can be made with this method.

Know Your Quad: H. Randall, ZS1HF. General dissertation on the origin of the Quad antenna and information on its characteristics.

Must Erection Without Tears: T. Cust, ZS1-22. Describes a method of easily erecting a guyed mast using a gin pole.

August 1968—

No technical articles.

"OZ MAGAZINE"

August 1968—

Converter for 1296 Mc.: Flemming Rasmussen. Describes a transistor converter using trough lines.

Receiver with Ceramic Filter: H. Siellerup Rasmussen. Describes a solid state receiver for the Amateur bands using ceramic filters in the i.f. stages.

"SHORT WAVE MAGAZINE"

June 1968—

Six Band C.W. Transmitter: Described as "a modernised version of a standard design"—incorporating rx pre-amplifier, break-in and fully key controlled. Runs about 100w. to 6140. V.h.f. Working by Meiser. Scatter. Terminology, procedure, method, equipment and example.

Some Gelsco VFO/Exciter Modifications: Some suggestions for improving the stability, h.f. band wide and note of transmitters using these popular units.

Vertical Aerial Systems for the Communication Bands: Materials, methods of mounting and a co-axial dipole for ten metres.

July 1968—

Practical Two Metre SSB Transceiver, Part 1. Design, circuitry, construction and alignment. 80w. on a QWV6/40.

Testing Silicon Diodes: Tells how to determine peak inverse voltage, etc.

Basic VFO for Multiband Operation. At first sight it looks a little like a Gelsco. Tubes used are 6C4 and 5763. Clapp oscillator circuit is used.

Station Control System: Ideas for circuit arrangement, describing a practical case.

Notes on Joystick Operation. Loading up, use of a.t.u. and s.w.r. indicator. This should interest some of those who have bought Joysticks.

Small Transistor Tx for Two Metres. Describes a small unit with an output of about 100 mW.

September 1968—

Command TX/PSU for Standby Operation: G6PG. Describes a small, 15w. two stage single band tx and 300v. 80 mA. power supply; for 1.8, 3.5 or 7 Mc.

Simplified Transceiver for the Two Metre Band: G6JUV. Author describes unit he built for 2 mhz from an old low band mobile and suggests how it can be adapted for 4 mhz. May appeal to 2 and 6 mhz men.

"RADIO COMMUNICATION"

June 1968—

1 Mc SSB Phasing Exciter Using PETS: G6MNG discusses the theoretical approach to the problem and then gives a practical solution. This article could be of major interest to v.h.f. h.b. addicts.

Reflexometers and Directional Power Meters: G6NJV goes into the theory of operation of these devices complete with the mathematics. He then describes a device which differs from the usual v.s.w.r. meter because it is not sensitive to changes in the operating frequency.

Miniature Wave Cabinets: G6JUV describes a simple method of making acceptable cabinets from readily available components with the

tools which will normally be available to the average Radio Amateur.

The British Trans-Arctic Expedition: G2FLB describes the hardships and problems encountered by the party which is at present attempting to walk across the ice from Point Barrow in North America to Spitzbergen. Previous attempts have failed to recognise that the ice is in constant motion and have walked against the current as it were. The present expedition is using the current to help them on their 3,800 mile journey on "Shank's Pony".

Technical Topics: In this issue Pat Hawker, G3VA, discusses on transistor repair jobs thyristor control circuits and the interference they can cause unless the equipment incorporating the thyristor is properly "suppressed" and shielded. A new type of transistor mixer, patented by CPTH-HB is described. This is covered by British Patent No. 1,104,928. Common collector configuration is used and although the circuit has practically unity gain, it is said to be very low noise and is not nearly so lossy as diodes. The circuit is said to overcome the transistor saturation problem. "Another Crystal Oscillator" circuit operating in the parallel resonance mode is described. Fundamentals between 1 and 20 Mc. is used.

Pat Hawker also discusses the articles which have recently appeared regarding some of the new developments in "Compact Aerials" such as "The Army Loop" described in "QST," March 1968.

July 1968—

A Simple Solid State Sideband Sender: W. B. Hartog, G3JEJ. They've gone all German in the title. A brief look indicates that this article contains some useful ideas for the man who wishes to "roll his own" in the face of all the opposition from the manufacturers. A Section of Co-Axial Connectors; Mrs. K. M. Priestley, G3KIW. The author describes most of the inexpensive type co-axial connectors available on world markets and tells of the advantages and disadvantages of some of them.

Technical Topics: This month Pat Hawker talks of the advantages of Morse, simple product modulator, new monolithic filters, the latest development in the crystal filter field. "The Modern VFO", an active antenna and various types of recirculating v.f.o. circuits such as the Sailer and Vaccar using PETS.

The Idea Behind GBZLO. GBZLO is the station the R.S.G.B. set up at the 1968 "City of London Festival". Sylvia Margolis discusses the concept and what is expected from the "advertising" that British Amateur Radio is receiving.

A Fresh Approach to the TVI Problem. Various ways of preventing spurious signals from being radiated are discussed and also methods for preventing "spurious Amateur signals" from being generated in various pieces of entertainment equipment.

September 1968—

Loop Aerials: G6NA. A discussion of loop aerial characteristics and their uses for transmitting and receiving.

A Simple Audio Oscillator and Pulse Generator: ZL2AMJ. Using parts of the type we can get in Australia, the author describes a simple wave oscillator with a frequency range 15 p.p.s. to 139 kc. output 5v. pp. sq. wave covers the same range and has a variable "modulating" rate.

Technical Topics: G3VA. This month Pat Hawker ranges from Transmitters to Modulators and Light Communication, n.b.f.m. and a.f. filters are by the way.

"DL-QTC"

September 1968—

Multiband Quad: D4VM. A different sort of quad. The elements each consist of two triangular closed loops on each end of the boom and the whole thing is fed by tuned feeders from a matching unit. Both ends are driven. For 20, 15 and 10 metres.

"QST"

July 1968—

The M.A.R.A.L. Antenna: K1KLM. This looks like a reasonably practical version of the "Army Loop" applied to mobile. It is built of rectangular down pipe and looks like an overgrown packrat.

Signal Light Drives: W6AGQ. Symbols, nomenclature and principles.

(Continued on next page)

Integrated Circuit Frequency Divider: K9CFZ. An application to the Amateur frequency standard.

The Chipboard: W6WYD. A simple experimental circuit board.

Some Ground Rules for Sweep Tube Linear Amp. Design: WICER. Four 6KD6s as π -triodes with individual bias adjustment for each tube to avoid purchasing a "saw" and matching them. 860v. input with 900 volts.

The Double Bazooka Antenna: W8TV. Broad-band dipole using co-axial construction.

August 1968—

The Connecticut Bond Box: WICER. Doug De Maw describes a solid state transmitter for 144 Mc Super-regen. rx and tx running about 4w. input.

A 65 Foot Crank Up: VE2EAS/W6. Quite a job for those who are really good with things mechanical.

Digital Counter with Teletype Print Out: W8RBN. ICs, etc., in a sophisticated piece of equipment.

The SSB Mark I: VE2EB. A simple transistor transmitter for 20 and 75 (80) metre sideband.

A Transceiver Monitor using Transistors: W8IBX. For those whose transceivers do not incorporate a monitor, this could be a handy gadget. Short and simple.

September 1968—

A Transistor Phone Rig for 1.8 Mc: WICER. Solid state for the "top band". Input power is 7-8 watts.

800 to 20,000 Metres: W8IKU. A simple transistorized converter for the v.l.f.

The C-Line Matcher: W6CKP/AGKFP. Simplified impedance matching on v.h.f.

A Tester for Crystals and Transistors: WINPG. The title describes it.

The Two Tailed Monster: W6ISQ. The recipe is to take one four element multiband quad and add tails to the boom to resonate it as a rotatable dipole on 40.

The 27Mc: K6LZM. Running 12 watts a.m. on 27 Mc. for 2 metres.

Notes on the Vacation Special: W2TFM. Describes as "a tunable filter for the BC454 and an improved 50w. transistor modulator for the 3500". There are still enough of the Commands around to interest VKs.

Inductance and Q of Modified Surplus Terrestrial Inductors: W3NQN. Something for the R.T.Y. boys.

General Purpose VFO: WICER. Solid state, of course.

Prefabricated Portable: W6YHT and W6ASF. Makes portable rigs from various modules which are readily available on the market.

The Serap Box: K2ENU. Describes some of the traps into which Amateurs can fall if they do not have proper test equipment to test the junk box and disposal items they propose to use.

"73 MAGAZINE"

July 1968—

Let's Build a Tower: VE1TG. Sturdy wooden construction tower.

Why Not a Tiling Tower? W6DL. With this method you won't.

40 Feet Non Conducting Skyhook: K1VBQ. Making a portable of phone pole.

Burn Protection: VE3BUE. A safe place for the hot soldering iron.

The Beam Pole: W7GEBJ. Another phone pole idea.

Tilt That Tower: W2AJW. Using the house for leverage.

Wash Trap Filter: Ives. Another idea to all the holes.

IC Audio Amplifier and Oscillator: W7AKS. ICs and a lot to play.

The New Tower: W2AGXT. Battling the tower inspector.

Some Audio Thoughts: W3KBM. Versatile module with a new type transformer.

DB: W8PAP. More on Crystal Etching.

K6GKP. Using readily available chemical.

August 1968—

Terminated Grid Linear Amplifier: W8IDS. Broad-bandable configuration. Two Elmac 4-400As for 2 kw. input. A little too large for Australians.

A Unique Transistorized DC/DC Converter: W6VJF. Converter using a conventional transformer. This article describes a converter using a c.t. step-down transformer from 117 to 120v. 30v. d.c. from a 12v. battery. The circuit used is a multivibrator amplifier arrangement which dispenses with the conventional saturating type transformer. This technique would probably work to provide 600v. from a 240v. type.

Photographic Printed Circuit Process: W6AYZ. Printed circuit etching made easy. Now that is interested in making their own?

A Model of DSB Conversion: K5LLI. An easy way to d.s.b. using a "balun" for broad-band feed. Seems good.

Basic HF Receiving Converter: W4U2M. Getting more from your h.f. receiver. Simple circuit using two twin triodes.

Three on 30 for 15: W4YVQ. \$15 three element beam for 30 mc. Seems practical, but involves using elements with some lightweight wooden members.

The Mini-Boom Quad: VE2FS. Efficient quad with spider array. Some handy ideas for an inexpensive easily made quad (three-band variety).

The Collinear Resurrected: W4IDVD. End fire array without sacrificing performance. A simple wire array for 30 mc with a gain of 7.7 db.

A Microphone Preamp: W2EEY/J. More speech power without distortion. Simple single transistor/diode affair built into a hand mike.

Review—The Heath IM-17 VTM: W2TQK. A versatile piece of test equipment. The writer reviews the Heath battery operated solid state voltmeter.

Handing: K6MVI. A veteran writer tells how. An article on how to write articles for Amateur magazines.

A Grounded Grid Linear Amplifier: W6WUI. 3 through 30 Mc. in five steps. Circuit suitable for 4Z27s or 813s. Cathode driven linear for 800 watts input.

September 1968—

Going VHF in the Mobile: W3HFE. Describes how to get the most out of both v.h.f. and mobile.

Communicator Reborn: W6HGX. Double conversion of the Gonset Communicator makes the unit more selective and useful.

12 Mc Amplifier: W4AJW. Although Frank C. Jones is an old timer, he describes solid state equipment using a FET for 432.

Quick Conversion: W6HGX. Describes how you can use obsolete v.t. tuners to quickly assemble Amateur band converters.

So You Think You're on Frequency: K. Sessions. Methods of checking frequency on the v.h.f. bands are discussed.

Parallel T Network Design: Jim Kyle. Seems that there is a wealth of ideas to be found.

The VK3ATN Moonbounce Rhombic: W2NSD. Wayne describes some of the tricks Ray got up to, to make two-way moonbounce contacts with the U.S.A.

6 Metre Exciter: W1KNI. A handful of transistors and a 6CL6 on 6.

Six Metre Transmitter: W2AJW. Using transistor tubes, junk b.c. rx and a few extras to produce a small solid state transmitter for 6.

Two Sidebands from the Two-er: W4KAE. Quick and easy d.s.b. on 2 mc.

"CQ"

July 1968—

Modulation Unlimited, Part 1: W3PHL. A two-part article which is completed in the "CQ" August issue. Describes methods of "super modulation", i.e. modulation which exceeds normal a.m. 100 per cent. figures on sensitive peaks, but not on negative peaks.

Covers the principles and circuit techniques necessary to exceed 100 per cent. modulation without the production of undesirable sidebands, direct substitution and splitters. The modified final power amplifier circuit can be used for c.w., a.m., d.s.b. and s.s.b. modes.

Vertical Antenna, Part 2: W3PHL. Deals with theory and practice of this type of antenna which the author claims has never previously been described in depth in an Amateur magazine.

The Drake Solid State VHF Equipment: W2AEF. Review of the equipment for v.h.f. offered to Amateurs by the Drake Co.

Heath Linear is a Good Amplifier: W2EEY/J. Describes the various types of distortion met with in s.s.b. operation and equipment design problems with regard to intermodulation distortion (i.m.d.) which is rarely specified in Amateur equipment.

Improved FM Operation: W8AUI. Describes how proper maintenance of two-way f.m. equipment can improve the number of contacts in mobile operation.

Solid State Methods: W3YKT. The whys and wherefores of coupling circuits in solid state i.f. amplifier design.

PSB—The Variable Capacitor: K1EUF. Describes a method of using v.v.c.s for shifting the frequencies in f.s.k. work.

A Salute to Mr. One-Sixty: W2EGS. A rundown on Stewart S. Perry, W1BB, who has been on the air since 1912, mostly on 160 mc. Used a QRP rig for 30 years. Par 3: W2AEF. Describes how to use a g.d.o. for Amateur work.

August 1968—

The SST SERIES: K9AJ/2. A series of small "Solid State Transceivers" for 10, 6 and 2 mc. Using super-regenerative detector rx's operating at very low power levels to minimise distortion from the oscillating detector. Sensitivity is about 1 μ V. This is followed by a commercial a.f. amplifier which is used also as the modulator. The transmitters run inputs of about 100 mw.

The DX-pedition: D. Miller, W9WNV. Part VII. The Miller story.

The QM Keyer Monitor: W8ZQM. A simple tube type keyer with a transistorised monitor incorporated.

By Permission of Her Majesty Queen Elizabeth II: Sylvia Margolis. The publicity officer for the R.S.G.B. describes the station sponsored by R.S.G.B. at the 1967 National Rally of the Caravan Club of Great Britain. Station operated under the call sign GB3CC.

Modulation, Part 2: Describes modifications made to Heathkit DX100 putting ideas into operation.

The Heathkit HW-100 Transceiver: "CQ" Review. This is Heath's low priced £240 (US) five-band unit which according to this reviewer gives a very good account of itself. After reading this story I feel that certainly wouldn't want to spend £360 (US) for the SB101.

Vertical Antenna, Part 3: Paul Lee continues his dissertation on this topic.

RF Feedback in Audio Compressors: K6SHA. Short article on elimination of r.f. feedback.

The Shesbox Symposium: W2EEY/J. This article has described two Shesbox's. The first in 1966 and Mark II. in "CQ" July 1967. This article describes methods of overcoming the various problems which have been encountered by builders of a linear which can be set to run inputs of from about 800w. to 2,000w. peak d.c. according to the number of tubes used in parallel.

The new 6L60 which has a special rating of 200w. for 30 sec., should be very suitable for this circuit. At this time and its competitors equivalent is now finding its way into many of the newer transceivers which are operated at 360w. input levels. There is a mistake on the circuit shown on p. 8.

SSB Reception With Signal Frequency Injection: VE7RKH. Seems to me like a new method of doing it the hard way.

A Home-Brew Broad-Band Transmitting Balun: W2EEY/J. The balun described is made from a length of co-ax wound on a plastic pipe. The other end of the co-ax is connected the same technique could be used with 75 ohm cable to give 75 ohm balanced to 75 ohm unbalanced conversion.

Wideband RF Pre-Amplifier: W6DYD. Describes a low noise broad-band FET/transistor amp. with a gain of 25 db. up to 15 Mc. with a noise figure of 2 to 3 db. Some people may be interested in this technique. My personal reaction is that one would lessen interference by using a tunable device.

Upgrading the SB-100: W6VHY. Modifying the Heath SB-100 to improve its a.v.c. system.

☆

A TRANSVERTER

(Continued from Page 6)

say another 12B77, and then have the 6CN6s in passive grid, or semi-passive grid.

No attempt has been made to use this transverter on 21 and 28 Mc. by bandswitching, but this should be fairly easy. The same crystal oscillator and buffer amplifier circuitry would be used, and the same crystal. You would have to switch the tuned circuits in the converter, the coil in the plate of the mixer, and the final tank coil.

All tuned circuits in the converter, the oscillator and the buffer are slug tuned. No coil data are given, except that all coils other than the final grid and final plate are on 7 mm. formers. Injection to the 807 is by 3 or 4 turns over the end of the 6AM6 plate coil.

I will be glad to answer any mail queries, provided that they are accompanied by a self addressed stamped envelope, and provided that you don't expect overnight service.

Publications Committee Report

At the November meeting correspondence was received from 8M2DQ, VKs 8AQ, 3UC, 3AMK, 5HI, 5RG, 7KJ, Nola Sturke, E. Foxon, W. Morgan, and LT081. Technical articles arrived from VKs 2FR, 2SA and 8ZNV. Due to the lack of figures, the financial position of "A.R." could not be ascertained accurately, but it is estimated that the position is reasonably satisfactory.

Efforts to increase advertising content are proving fruitful, the advertising representatives having already signed up a number of new advertisers and recovered some of those lost several years back. A major effort will be made in this direction during November. A review of technical material on hand revealed sufficient available to see us through to the February issue, and extra material, particularly short articles, are badly needed.

Progressive results of the November questionnaire were discussed and a very good initial response reported. No replies had been received from VK2, but this was thought to be due to the postal strike in N.S.W. having delayed the delivery of the November issue. Over 200 replies were received within 48 hours of "A.R." being mailed. Initial sorting has commenced, but until many more replies are received, no attempt will be made to compile statistics.

At the suggestion of the VK3 Divisional Council, the committee gave consideration to making token payments for technical articles published. After lengthy discussion, it was agreed that although the suggestion held considerable merit and in fact conformed to the wishes of the committee as outlined nearly three years ago, it would be better held over for a minimum period of six months, in order to see what additional income (if any) we can acquire. In the meantime, we will continue to make the annual awards for selected articles, as we have done in previous years.

The value of the monthly Publications Committee Report was questioned, and the general opinion was that the time compiling it could be better spent as it has to be done during our busiest time of the month. It was, therefore, decided that despite the fact that it has been produced as the result of a Federal Convention policy motion some years ago, the report would be discontinued as from this issue. Technical articles and correspondence will be acknowledged by mail in due course, with the exception of any correspondence published in the magazine, for which no acknowledgment will be sent.

All Call Book orders have been fulfilled. Any Division or club requiring additional copies should contact us, as we have a small surplus available.

SILENT KEYS

It is with deep regret that we record the passing of the following Amateurs:

VK1PI—Les Pitts
VK2AYA—G. A. Ahlstrom
VK2AYB—Sid Burton
VK3VO—Raymond Clark

TESLA EQUIPMENT IN AUST.

The internationally famous Tesla electronic equipment is now available in Australia through Charmac Industries Pty. Ltd., Eltham, Vic.

Founded in Czechoslovakia 60 years ago, the Tesla company now employs 75,000 people in 50 factories and manufactures heavy electrical and telecommunications equipment.

Charmac Australian sales manager, Les Baker, advised "A.R." that in addition to the range of Tesla tape recorders and audio amplifiers, they would distribute Tesla components, and Agia tape which had been found most suitable for use with Tesla recorders.

An associate company, Audio-Lec of Australia Pty. Ltd., will distribute the Italian made "Incis" audio equipment.

W.I.A. D.X.C.C.

Listed below are the highest twelve members in each section. Position in the list is determined by the first number shown. The first number represents the participant's total countries less any credits given for deleted countries. The second number shown represents the total D.X.C.C. credits given, including deleted countries. Where totals are the same, listings will be alphabetical by call sign.

Credits for new members and those whose totals have been amended are also shown.

PHONE

VK3MS	315/328	VK1AB	286/314
VK3AHQ	312/326	VK4P	282/301
VK6RU	307/322	VK4TY	275/278
VK4ER	304/322	VK3TL	271/277
VK6MK	304/322	VK1APK	269/274
VK3JZ	303/320	VK2AAK	268/273

New Members:

Cert. No. 91	VK3WD	106/106
Cert. No. 92	VK3VK	152/153

Amendments:

VK4KS	288/283	VK4PX	178/179
-------	---------	-------	---------

C.W.

VK2QL	300/322	VK3YL	266/263
VK3AHQ	292/306	VK3ARX	266/275
VK3CK	289/312	VK6RU	266/289
VK4FJ	289/313	VK1APK	265/273
VK2AGH	282/286	VK3NC	264/277
VK4IR	276/296	VK3XB	263/277

Amendment:

VK4PX	102/106
-------	---------

OPEN

VK2AGH	311/331	VK4TY	301/315
VK4IR	309/333	VK4FJ	290/320
VK6RU	309/334	VK3ARX	280/289
VK6MK	305/324	VK3TL	271/273
VK2VN	304/321	VK2APK	266/266
VK2EO	302/325	VK3XB	260/274

New Member:

Cert. No. 114	VK3EU	107/107
---------------	-------	---------

Amendments:

VK4KS	274/293	VK4PX	200/205
-------	---------	-------	---------

World Admin. Space Radio Communications Conference

Of three resolutions published by the I.T.U., the following extract is worthy of note. Reference is made to this in Federal Comment (this issue).

"... The second resolution, which is less important, calls for the convening of a World Administrative Space Radio Communications Conference to take place towards the end of 1970 or the beginning of 1971 for a duration of about five weeks.

"The agenda of this conference is to include in particular the following items:

1. To revise existing administrative and technical regulations and adopt such new provisions as necessary for the space radio services and the radio-astronomy service which will ensure the efficient use of the spectrum;
2. To consider, and revise as necessary, the provisions of the Radio Regulations pertaining to the Aeronautical Mobile and the Maritime Mobile Services and to navigation in so far as the use of space techniques is concerned;
3. To consider and provide as far as possible, additional radio frequency allocations for the space radio services;
4. To revise and supplement as appropriate the existing technical criteria for frequency sharing between space and terrestrial systems and establish criteria for sharing between satellite systems.

"In the same resolution, Administrations are invited to submit proposals on the agenda of this Conference. On the basis of these proposals, which will be presented in a report by the Secretary-General, the 24th Session of the Administrative Council will decide on the detailed agenda, date, duration and place of the World Administrative Space Radio Communications Conference."

VHF SSB

YAesu MUSEN

FTV-650 Six Metre Transverter

For transmitting, takes low level 28-30 Mc. excitation from an SSB transmitter or transceiver to provide output on the 50-54 Mc. band. For reception, covers 50-54 Mc. with I.F. output on 28-30 Mc.

WRITE FOR DETAILS

Sole Aust. Agents:

BAIL ELECTRONIC SERVICES
60 Shannon St., Box Hill North, Vic. 3129. Phone 89-2213

Rep. in N.S.W.:

A. J. Bruce-Smith
47 Hyman St., Tamworth, 2340
Phone (STD 067) 66-1010

For Reliable Connections

RESIN CORE SOLDER
O. T. LEMPRIERE & CO. LIMITED

Head Office: 31-41 Bowden St., Alexandria, N.S.W., 2015
and at Melbourne, Brisbane, Adelaide, Perth, Newcastle



Sub-Editor: PETER NESBIT, VK3APN
32 The Grange, East Malvern, Vic., 3145

BAND NEWS

28 Mc.: From Don VK3AKN comes a very comprehensive rundown of conditions on 10 mc. Here goes: "At 0700 E.A.S.T. the bands open to the East Coast of the U.S.A. The opening moves across the States until 1100, when Ws peaks. The Ws generally fade out at about 1200. JAs and UOs start about 0600 and last until dark at 7 p.m. UAs sneaks through about 1100, although I did work one once at 7 a.m. UL7/UL8, etc., start at about 1800, and UDE/UA3, etc., picks up around 1900. DM3IGY comes through about the same time. "Western Europe (DL, LA, SM, etc.) comes through around 1800. Africans start around this time, although sometimes as early as 1600. Gs, Fs about 7 p.m. and then general QRM from all over Europe. The band usually fades at 9 p.m. or so. If it stays open until 11 p.m., as it does sometimes, then Caribbean stations come through on long path and have worked KV4CI often at 1000. "Sometimes when auras is in effect, can work Eur./U.S.A. stations with the beam pointing due north. The auras bounce often causes good TD signals to change to TS, the effect sounds quite strange."

VQCCQ, who is active 15/20/40 mc as well, reported 2625 at 1200.
ST2B, 15/22z. Has been active 1402z at 21z; also 2650 at 1237z.
TLAGI—2650 at 1930z. QSL via VE2DQY.
Q7WVW 2653 at 2010z. QSL to Box 453, Bantyre.
9L1KZ Sierra Leone 28517 at 19z.
AP2MR 2852 0943. Has gear for 80 mc. QSL via VESACD.
9N1MM, an s.s.b. veteran of 15 and 20 mc, 2655/576 around 09/11z. QSL via W3KVP.
Q7WVW from Crete 28587 at 1030z. QSL via K3EUR.
T3BUR 28620 at 14z. QSLs via WABRE.

21 Mc.: YAIHD 21310 at 1230z; QSL via DJ1HJ.
AP2MR 21310 (wonder if his last name is Place), 21325 at 12z.
VP2AA Antigua 21286 at 2233z. QSL via VEGAD.
VP2AD, DJA, Dominica 21256/261 respectively at 2150z.
CEADAE from Easter Island 21336 at 22z.
VO1J in the Reg. of Sonora 21336 at 1930z.
VS7TJ active from Brunel, week-ends 21300 at 12z.
AP2HJ and W4UDE/AP will be active 21305 at 12z.
FB2XX Kerguelen Isl. 21075 at 0812 and 1310z.
TASAR, "Lumar" KTSAD, QRV daily 21040 and 21055 at 1235z. 15-20z. Plans to stay there until Feb. next year. QSL via WATGGA.
LAST Tromso Archipelago 21328 at 08z, 21310 at 12z.

LAIT Vesterlen Isl., 21336 at 0832z.
LGLSL reported on 21065 at 12z. QSL via LAATY.
SP2BK Ken is active 21355/270 at 0823/1148z respectively. QSL via WHNKH.
HS2ZZ, Chuck reported 21322 at 1316z. QSL via K2VJ.
TU2AX 21325 at 2215z. Box 4066, Abidjan.
5ZAKK on 21335 at 2205z. QSL via K1SLZ.
9K2CC 21313 at 1130z. QSL via K9CSM.
SA1AM from Antigua 21309 at 1130z.
LX1MH 21325 at 1339z. KM6CR 21392 at 02z.
5N2AAU 21283 at 21z, QSL via WABUFW.
E25JY 21284 at 1400z.
N2PMBR from Muscat and Oman, 21325 at 1202z.

CR3AD on 21095 c.w. at 1230z.
11 Mc.: OH8AA Aaland Isl., 14045 at 0850z.
Q7WVW from Antigua 14202 at 02z. QSL via VPKRK and VPKAK on Falkland Is. Both 14022 at 02z. QSLs for VPKRK via KJ2KY.
FOC 14029 at 0500z. 5-20z. 1402z at 1135z.
Gibraltari ZBZA on 14085 at 21z. ZBZY 14025 at 2213z.
Gunatanmo Bay: KG4AM, 14223 at 06z.
AP2HJ is being active on 14002 at 1424z.
AP2DI and WAUDF/AP both active from East Pakistan, 14050/205 12-14z.
French Guyana: FYTYY 14050 2230z, also on 5-20z. FYTYY 14050 2230z, also on 5-20z. FYTYY 14050 2230z, also on 5-20z.
Seychelles: VQURF has been active 14048 at 12z and 13z.
ZK1AA, Stuart has been active again from Cook Isl., 14218 at 04z.
JT4AH has shown up 14028 at 15z.
N2PMBR is now back as V58AG. CR3AK active 14195 16-18z.

FB5WW has been active from Crozet Isl., 14210 0615z.

V57TJ, Slim is still active, 14171/216 between 11 and 12z. QSL via Box 308, Brunel.
CR3SP and CR3IV are QRV for Pacific stations, 14170 Sundays 0530-0900z.
Victor CR3LJ is also QRV for Pacific stations daily 14155 at 0600-0730z.

FH8CD uses 14125. Andre skeds FB5WW and SUREB daily at 1530z.
UAIKPT Noryia Zemlya, 14052 at 0745z.
F4IE/W8W will be operating until Dec. 2 on 14 mc at 17-18z.

9X5MF/EA0 14190 0645z: QSL to HB Bureau.
9X5MF/EA0 14182 2123z: QSL via HB9MQ. Fernando P is rumored to be breaking away from Pacific Guinea, so it is likely to have a new prefix soon.

OX3AP (Harry, WBEM/JC), 14229 at 21-23 and 03-30z. The lost logs of June 16/70 67 have now been recovered. If anyone who missed getting a QSL during this period, please send s.s.b. plus two IRCs to H. Leggans, Box 12, R.C.A.S.-B.M.E.W.S., A.P.O., N.Y., 09023.

OX3AP (Scotty) 14179 0812z. QSL via WACUC.
TF2WLC 14260 0815z, often FRV 21355 also. QSL via WA4PFD.

ZK3ZC, 14260, 14260 14270 Fridays at 0430z.
8E1J, Peter, 14075 at 0120z. P.O. Box 557, Georgetown.

BV2A, Tim operates 14028, usually 12-16z, hopes to be QRV during contacts. His address is: Tim S. H. Chen, 6144 Hsin Sheng Road, Section 1, Taipei, Rep. of China.

14028, 14028 14179 0812z. QSL via WACUC.
ST5AD "Alban" is often active 14250 around 07/08z.

7 Mc.: D1UHF, Earl hopes to be QRV with 2 kw and 2-40 mc quad by Nov. and is trying for a D.X.C.C. on 40 mc and will be planning to arrange skeds. Also hopes to work VK/ZL on 6 mc using at 11-01z, yaq!
VU2LO has been active near the band edge 7001 with a good signal. Reported at 1235 and 15z.

KR3EA with a good signal on 7020 at 1530z working JAs.

T12PZ, Jose is back on 40 mc after a temporary absence. Reported on 7010 at 06/07z.

HI3PC is on almost every evening 7005-10 around 06-10z.

PY4DS shows up occasionally, 7025 at 0745z. Name is Ram.

AP3HQ has been heard/worked several times recently. He stays very close to the band edge and sneaks right off about one per minute. 7001 at 1230/1545z.

HM45W 7013 at 1130z.
OM2IZZ, John, calling CQ VK/ZL 7005 at 0725z (long path).

VU2JJA, Joe requests QSLs via WACTN, 7010 at 0450z.

OA4UO, Ted works 40-10 mc. 7015 at 1043z.

8.5 Mc.: ZK1AA, Stuart is QRV 3800 a.m. daily 0830z, with Harry ZK3AE.

GM3XPQ, Sheldan Isl. (north of Scotland), 3795 at 22z. Presumably he would come on earlier for skeds if requested.

BV1PA worked first of all on 40 mc, then transferred to 3508 where signals were 55 both ways at 1305z.

K4ZRM 3820 at 0904z.

K5SCC, who is on 80 mc now, says he hopes to be active on 160 mc very soon.

1.8 Mc.: GM3XPQ, George reported on 1876 s.s.b. at 2030z.

WV3XO is at present visiting the Caribbeans and is an enthusiastic 160 mc man. So far he has been to KV4 and VP2, and plans many more good ones before he returns to the States. He usually uses 1854, but has rocks down to 1802.

Other recent DX-peditions using 160 mc have been ZF1EP and F0JMM.
Future plans for 160 mc trans-Pacific tests (see last month's "A.R.") there is a rider that the times given are not rigid. VK/ZL stations are asked to start around 1300z. Trans-Atlantic DX Tests are scheduled for Dec. 1, 5, 29; Jan. 12; Feb. 2, 6. Calling procedures are the same as in the trans-Pacific tests, with European stations calling during the odd five minute periods, 1905-10, 1915-20, etc.

ASSORTED

S.s.b. interference from Spanish speaking stations in the c.w. section of 20 mc has been increasing lately. Additionally several instances of "burr" have been cutting deep to places. A.R.R.L. has a special section which would like to obtain calls, times and freqs. of stations so that they can be taken.
The Canadian DX-pedition which is presently doing so well for itself under numerous Pacific calls, 14170 and 14200 on 0945 to 1600z; 21290-300 from 2200 to 2320z; and 28530 around 23z.

9K2BV hopes to be operating from the Kuwait/Saudi Arabia Neutral Zone soon, if possible.

FOB3B is a French Scientist attached to a nuclear testing station on Tuamotu Archipelago in the Pacific. 14195/15 0630/0730z.
HRC: s.s.b. a.e. plus five IRCs to Box 541, Hong Kong.

WG4GSG was a special station from Gogeechee Falls, Statesboro, Georgia. Special QSLs via W4QDQ.

W4QVJ is not QSL manager for CE0Z1/AM, only for Ed's operation of CE0Z1 Oct. 63.

7 Mc. VK3BH is reported to be erecting a 30 ft. fixed quad on 40 mc, heading to Europe!! (Gulp!!)

Starting Feb. 1, Gus WB2PD plans to set out another month's worth of DX-peditions which may last up to five years, funds permitting, and run along lines to make the sport of DXing what it was a few years ago. Gus will operate a c.w./s.s.b. 160-19 mc. All donations as soon as possible to QSL mgr. WAECI, cheques payable to World-Wide Radio Propagation Study Association.

U1A: Special call sign allotted to a group of Leningrad operators for the "CQ" W.W. Test.

VK3XK states that he is not intending anything on 160 mc, but 1500 others are interested in Amateur activities, and they will be licensed.

Next Feb. WB6PO is going to Norfolk Is. as VK2BPO/9.

DX3DY QSLs are now acceptable for DXCC credit.

Art VK4PK writes on licensing in Indonesia from information sent by YB4AR: There is a new method of licensing in Indonesia. It will be sent direct. There are only 18 international licensees at present using the prefix of YB. The holder of YB IDP, or 1500 others, are interested in Amateur activities, and they will be licensed. Avoid working YC and YD stations as these are not international and will not QSL. Until three months ago, there had been no legitimate Amateur activity. Any stations heard using PK prefix are pirates. The call areas are: YB1D, YB2D, YB3D, YB1012D, YB1013D,

V.H.F. NOTES

Well another year is rapidly growing to a close, the DX activity is on the increase, both on 6 and 2 metres, but alas, no reports of any activity on 432 Mc. Surely there is not the problem of t.v. on this band like there is on both 6 and 2 mcs. Anyhow, enough of the moaning, now on to a few brighter subjects.

First, the 1968-69 Ross A. Hull V.h.f. Memorial Contest starts on Saturday, 7th December, 1968, and continues until Sunday, 12th January, 1969.

Secondly, the Festive Season is near, so I would like to wish you all a Very Merry Christmas. Very Prosperous New Year, and may your Xmas stockings be filled with some rare DX. TX, Cyril VK3ZCK.

P.S.—Many thanks to those who have contributed to this column over the past year, and I hope that you will continue to do so in 1969.

VICTORIA

Reports indicate that this coming DX season will be one of the best experienced for some years.

Six Metres.—Band openings which took place in late October enabled all States to work JAs at very good strength. The number of stations using 50-55 Mc. will be interested to know that the VK6s also operate in this band and are anxious to work into VK, while the JAs usually use 50-51.5 with the main activity between 1500 and 2000 E.A.S.T.

Two Metres.—For those who are only on this band these are also looking up, with openings to VK4, 2, 5 and 7 being quite common, but the occasional opening to VK4 will increase the DX activity on this band.

The VK3 V.h.f. Project Group has almost completed the 2 metre converter, a companion to the very popular 6 metre one which was published in "A.R." about 12 months ago.

Don't forget the Ross A. Hull V.h.f. Contest which starts on 7th December and continues until 12th January, 1969. TX, Robert VK3AUR.

Gippsland.—During the recent C.F.A. exercise much use was made of the 2 mcs f.m. channels, with the assistance of a 52.925 Mc.

f.m. link between Thorpdale and Mirboo North and h.f. and s.s.b. On the same week-end David VK3DY, from Maffra, and George VK-3ZCZ, from Morwell, attended the V.h.f. Convention at Bendigo. This seemed to start the ball rolling as far as the DX goes, for since then some very good openings have occurred on 2 mcs, mainly to VK5 and VK1, with a fair sprinkling of the northern VK3s.

WESTERN AUSTRALIA

The new committee of the West Australian V.h.f. Group are: President, John VK3ZGL; Vice-President, Harry VK6HP; Secretary, Edwin VK6ZAN; Treasurer, Cedric VK6CD/T; Committee, Neville Chamberlain, Wayne VK6ZDD and Tom VK6ZAF; Bulletin Editor, Harry VK-6HP; Technical Editor, Tom VK6ZAF; Bulletin Circulation, Roy VK6RY, Glen VK6ZFH, Bob VK6ZFY; Broadcast Officers, Kevin VK-6ZCB/T and Don VK6HK; Oscar Co-ordinator, Don VK6HK; QSL Officer, Laurie VK6ZEA; V.h.f. Records, Rollo VK6SO; Beacon Officer, Tony VK6ZDT; Press Correspondent, Percy VK6ZDC; Auditors, John VK6TO and Ray VK6KU.

The club station VK6SVF is operated by D. E. Cook, VK6AV, and runs beacons on 52.005, 145.00 and 432.50 Mc. Another beacon should be in operation by the time these notes are being read. This is at Albany and will be on 144.5 Mc. with a beam on Adelaide and another on Perth. The power is about 60w. to a converted Pye base station and is sited on a 1,500 foot hill with a good path to the East.

Notes used in this State are: 52.586, 52.662, 53.8 and 52.020 Mc., all a.m., plus 52.656 and 146.00 Mc., both f.m., 10, Percy VK6ZDC/T.

NORTHERN TERRITORY

Activity from the Darwin area should be much greater this year, now that active Amateurs include Doug VK6SE, Jim ex VK6ZJ and myself (Bruce VK6AZ, ex VK6AZG). We are working on a Radio Booster Station at Cox Peninsula for Radio Australia. I hope to establish regular schedules on 20 and 40 metres with either VK6BA or VK3YO and possibly with VK6AZK, with all of whom I used to work. TX, Bruce VK6AZ.

NATIONAL FIELD DAY

The John Moyle Memorial National Field Day Contest, 1969, will be held from 0600 G.M.T., 1st February, 1969, to 0800 G.M.T., 2nd February, 1969.

The rules for this contest will be published in the next issue of "A.R."

STATE INTRUDER WATCH CO-ORDINATORS


New South Wales—
W. H. R. Treloar, VK2RPZ, 23/8 Fullerton St., Woolahra, N.S.W., 2025.
Victoria—
M. P. Davis, VK3ANG, 144 Tramway Pde., Besenmaris, Vic., 3193.
Queensland—
Ken. Kenny, 19 Lithgow St., Wynnum Cen., North, Qld., 4178.
South Australia—
W. J. Bulling, VK5KK, 297 Goodwood St., Kings Park, S.A., 5034.
Western Australia—
G. Allen, 283 Amelia St., Balga, W.A., 6061.
Tasmania—
D. H. Kelly, VK7DK, 56 Upper Brougham St., Launceston, Tas., 7250.

CONTEST CALENDAR

Until 31st Dec.: Concurso Mexico 1968 (L.R.E.)
7th Dec., 1968, to 15th Jan., 1969: Ross A. Hull VHF Contest (W.I.A.)
1st and 2nd Feb., 1969: John Moyle Memorial National Field Day (W.I.A.)
1st and 2nd Feb., 1969: 35th A.R.R.L. DX Test (Phone Section), first week-end.
1st and 10th Feb., 1969: A.R.R.L. Novice Round-up (C.W. Section), first week-end.
15th and 16th Feb., 1969: 35th A.R.R.L. DX Test 1st and 2nd Mar.: 35th A.R.R.L. DX Test (Phone Section), second week-end.
8th and 9th Mar.: 32nd B.E.R.U. Contest (I.S.G.B.).

PREDICTION CHARTS FOR DECEMBER 1968

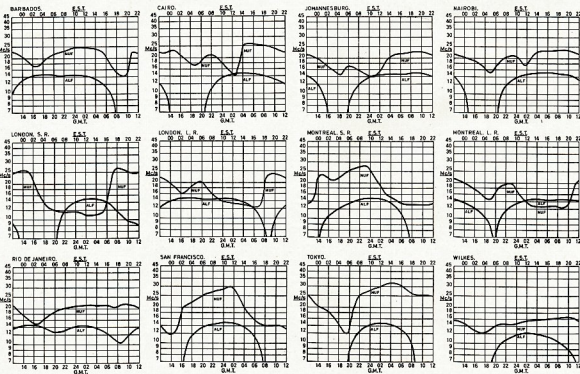(Prediction Charts by courtesy of Ionospheric Prediction Service)



Correspondence

Any opinion expressed under this heading is the individual opinion of the writer and does not necessarily coincide with that of the Publishers.

S.W.R. INDICATOR CORRESPONDENCE

Editor "A.R." Dear Sir,
In company with VK1JE (October issue of "A.R.") I thought that all who had gone beyond elementary electronics had discarded the belief in a rush along a conductor akin to the electric fluid postulated by very early scientists. Turning to page 34 of the October issue of "A.R." I read with amazement an advertisement for a Toroid Balun containing the statement "this device also prevents the wave which has been contained within the cable from tending to 'spillover' the extreme end and travelling back over the outer screen of the cable". Apparently there is still need to "labour the point" and carry the gospel of rational thought to the electronic heathens.

Listening recently to an Amateur station QSO I heard one remark that he was having trouble with reflected power, which, apparently having no other place to go on return from his mismatched antenna was dissipating itself on the plate of his final amplifier, causing considerable heating. Being so deeply immersed in the gobbledygook of standing waves and reflected power, this unfortunate station owner did not know that his badly mismatched transmission line was presenting so high a positive reactance to resonance, hence the adverse effect of the negative reactance in the output of the final stage pi network, preventing it from the ability to resonate, hence the excessive heating. Missionary work must continue in attempts to dissipate the fairy tale fogs which cloud many Amateur minds.

The diagrams indicating diode current flow are for instantaneous conditions occurring with non-reactive resistive external loads for which the internal meter line terminating loads have been adjusted to balance the inductive and electrostatic (current and voltage) components so that equal magnitude potentials are generated at the diode terminals. When these are equal and opposite in phase, no current flows through the diode. If the external load possesses positive or negative reactance in addition to resistance there will be a phase difference between magnetic and electrostatic components and the resultant two meter readings may be evaluated as indicating a reflected wave.

FOR SALE

PYE RANGER, 50 watt, 60 KC., Base Station, Model PTCA-1, 215, 215, 215.
PYE RANGER, 25 watt, 80 KC., Base Station. Both sets are complete and in working order. Best offer to—

GEM TAXI CO-OP. LTD.
2 THAMES ST., WEST HEIDELBERG, VIC., 3001
Phones: 45-2665 or 45-7115

CIRCUIT BOARDS

NOW AT REDUCED PRICES

1 to 99. 15c per transistor; 160 to 499, 12c; 500 and over, 10c. Diodes, etc., free. Technical details supplied. Minimum order \$2.00.

W.I.A. (TASMANIAN DIVISION)

Box 851J, G.P.O., Hobart, Tas., 7001

Stockists of Radio and Electronic Components for the Amateur Constructor and Hobbyist

First Ring, Write or Call on
WILLIAM WILLIS & Co. Pty. Ltd.

430 Elizabeth St., Melbourne, Vic. 34-6539

Repairs to Receivers, Transmitters; constructing and testing; xtal conv., any frequency; Q5-ers, R9-ers, and transistorised equipment.

ECCLESTON ELECTRONICS

146a Cotham Rd., Kew, Vic. Ph. 80-3777

In practical operation the meters indicate the summation of multi-million rectified pulses. The nominal directions of flow of current in the two diagrams cover only one cycle. When the power passes through the meter, the "calibrate" meter will always indicate. Only under conditions of resistive mismatch, and/or reactive loading will the meter in the so-called reflected power position give an indication.

Recently I had the pleasure of a conducted tour by VK2DO over the 330,000 volt three-phase distributing centre at Yass and stood beside three enormous 16,000 k.v. transformers employed for correcting the leading power factor due to capacitance of the long line from the Summit power station. An incident that passed through my mind. Had the Snowy Mountain electrical engineers followed the orthodox philosophy of Amateur Radio station owners the attempted solution to the power factor problem might have been the construction of a Gargantuan sized S.W.R. meter and accompanying "Match-Box" at the Mt. Kosciuszko end of the line!!!

Amateur Radio operators would be well advised to think in terms of power factor and reactance in dealing with transmitters and equipment. The same principles as applied to 50 cycles engineering still hold true at millions of cycles per second if care is taken in handling the many more zeros in the calculation.

—J. G. Reed, VK2JR.

THE AMATEUR—HIS SKILL AND STATUS

Editor "A.R." Dear Sir,

In reading the preface to the article on a.s.b. construction by our worthy brother VK2AOU, I feel that the question arises in the mind of the reader as to the Amateur and his skill and status. Not all have the skill or time of the writer, nor do they possess his flare for design and electronic engineering. The P.M. Dept. asks of the potential Amateur that he shows some knowledge of the art on theory, and sets out to work on his own. It is the writer's heart of mind that I have heard of. Until such demand is made on the part of the P.M.G., we shall have to be prepared to receive to our ranks hundreds of Amateurs who while equipped with the theory of the theory of radio and electronics, are quite incapable of handling a soldering iron and side cutters. Proof of this is the fact that dealers in standard equipment are still in business, and for this service many Amateurs are grateful. One who has the technique and skill to "roll their own", as VK2AOU puts it, should not be too smug or self-righteous, but be prepared to recognise the hundreds of excellent Amateurs who have not the same ability at the bench.

I also presume that VK2AOU does not grind his own crystals, and is not above purchasing the component parts he puts together. I can argue his argument to its logical conclusion, and he would scorn the assistance of all technical experts. Given another year, and what he is building today will be a crudity, and part at least of what he will build, will be constructed under a microscope. Technical advances will get far beyond the average Amateur and his workbench, and few Amateurs will have the technical ability to fabricate. Highly developed technical knowledge, however, will be quite another thing, and cannot be denied. The same might be said of today.

I am not one of the "new breed" mentioned, but look back to the days when all equipment had to be built in the shack and fixed components made one's own. The day when coils and spark coils had to be wound by hand. Today, however, there is a different situation, and the day goes on. The day when the assembly of purchased components. But the old men of radio who lathed parts for their switches, and made all parts to the last detail, do not seem the men of today who fling prefabricated parts together. It is all a matter of comparison and a little charity.

To such men who have the skill, I say my their shadows grow ever longer. It means leave the less skilled Amateurs to enjoy their hobby as they know best.

—"Harry," VK2HT.

R.T.T.Y.

Editor "A.R." Dear Sir,
On 6th October a group of enthusiasts met and formed the Queensland Amateur Radio Teleprinter Group, which is to be known as the "QART" group.

It was resolved to advise others who may be interested in or concerned with the group activities. The group is proposed to operate on a local net frequency of 144.53 Mc. and also on 14.075-14.100 Mc. and 21.075-21.100 Mc., at times scheduled for mutual convenience with overseas operators. Information of activity on other bands is sought.

Predominately British Creed page printers will be used on the American 80 standard.

Information on any r.t.t.y. equipment and parts is sought, particularly tape equipment. Licensed operators in the group are VK2ZGL, VK4ZNP, VK4NP, VK4AL, and VK4PJ, all members of the Wireless Institute of Australia.

Communication with overseas and interstate r.t.t.y. groups is welcomed and overseas acknowledgments and comments are sought.

For the group,

—Peter H. Brown, VK4PJ.

CONTACTS WITH VK

Selama Estate Group,
Serdang, Kedah, Malaysia.

Editor "A.R." Dear Sir,

As I contact Australia fairly frequently I keep a check list of VK stations worked for the first time. I might say that by no means do I work exclusively to Australia, and due to never having enjoyed a proper 24-hour electricity supply at any time out here, my Amateur hours are often limited.

Thus it was with some surprise on checking up that I find that yesterday a QSO with VK2DO resulted in my 1,000th VK station worked on phone.

I thought this was pretty good and would have been proud to count many of the stations may have now changed their calls or no longer on the air and many were in the old VK42 a.m. days. But it has been a pleasant surprise to me to recently meet again now newly on a.s.b. so many of the old VK stations which I used to work on.

The distribution works out as follows: VK1, 19 stations worked; VK2, 246; VK3, 288; VK4, 114; VK5, 138; VK6, 107; VK7, 22; VK8, 10; VK9, 42; VK10, 20; total of 1,000. QSL cards received from just under 500 stations.

Thus very much to all these Amateurs for so many splendid QSOs which have given me much pleasure and I hope that we will be able to work all for many years to come.

—James C. Fershouse, 9B2DQZ, ex 952DQZ.
P.S.—Any estimate of how many active VK stations there are on the h.f. bands? [Can anybody help.—Ed.]

ADVERTISEMENTS

Minimum \$1 for forty words.

Extra words, 3 cents each.

HAMADS WILL NOT BE PUBLISHED UNLESS ACCOMPANIED BY REMITTANCE.

Advertisements under this heading will be accepted only from Amateurs and S.W.'s. The Publishers reserve the right to reject any advertising which, in their opinion, is of a commercial nature. Ads must be received at P.O. 36, East Melbourne, Vic., 3002, by 5th of the month and remittance must accompany the advertisement.

FOR SALE: Galaxy Accessories, AC Power Supply 400-1500 100 kc. Xtal Calibrator \$7.50; Remote 400-555 Mc. GAW-12AT, \$30. Money 30 other Transmitters, with SWL, 1200 Hz. Frequency S8, Three xtal speed compressor, 8 in. speaker, h/phone o/p in 1 unit, \$5. 800 Secondary, VK8S5, Everest Ave., Morphettville, S.A., Phone 55-7538.

SALE: Special Receivers for SW's (four). All equipped with 1000 Hz. SW Meter, Noise Limers, etc. and in first class condition. Two at \$60, one at \$70, one at \$120. H. L. Roach, 28 Foster Avenue, Glenhilly, Vic. Phone 58-3757.

WANTED: Bendix Frequency Meter with AC Power Supply. Details to P.O. Box 57, Raymond Terrace, N.S.W., 2324.

WANTED: Circuit Diagram for AR88 Communications Receiver. If need be, will pay for circuit and parts. Copy made after contact with Capt. VK2J1, C/o. Telephone Exch., Pielke, Old., 4655.

WANTED: Commercial or equivalent A.C. P.S.U. for the ANAR113 Tx. also manual. Also an unmodified AFB Rx and a 12V vibrator Power Supply, 9 Bab. 7000, Yarraville, Vic. Phone 65-5313.

WANTED: Teleprinter Tape Repetitor and Tape Recorder. Call Graham, 864, or Phone 62-1351. Box 81, Albion, Brisbane, Old., or Phone 62-1351.

WANTED TO SELL: K.W. Viceroy S8B Transmitter and Power Supply. Nearest offer \$200. G. Bellas, 404 Geelong Road, West Footscray, Vic., 3012.



SPECIFICATIONS:

Frequency:	80m Band	3.5-4.0 MHz
	40m Band	7.0-7.5 MHz
	20m Band	14.0-14.6 MHz
	15m Band	21.0-21.6 MHz
	10m A Band	28.0-28.6 MHz
	10m B Band	28.5-29.1 MHz
	10m C Band	29.1-29.7 MHz

Communication Method: SSB (A3J)
AM (A 3H)
CW (A1)

Maximum Input Power: (Xmitter final stage)
200W (PEP)

Standard Input Power: (Xmitter final stage)
180W (PEP) 120W on 28 MHz band only

Antenna Input Impedance: 50-75 ohm

Carrier Suppression Ratio: More than 40 dB

Single Side Band Ratio: More than 40 dB

Mic. Input Impedance: High Impedance
(dynamic or crystal mic. recommended)

Xmitter Audio Frequency Characteristics:
300-3,000 Hz (-6 dB)

Receiver Sensitivity: 1µV S/N 10 dB
(14 MHz)

Receiver Selectivity: 2.7 kHz (-6 dB)
5.0 kHz (-55 dB)

Spurious Rejection Ratio: More than 45 dB

Image Ratio: More than 60 dB

Undistorted Power Output: More than 1W

Receiver Output Impedance:
SP 500 ohm
PHONE 8 ohm

Power Consumption (using PS-500AC):
450W (At maximum power output)
250W (Receiving Mode)

Tubes and Transistors used:
17 TUBES, 3 TRANSISTORS, 15 DIODES

Dimensions: W: 13 1/4"; H: 8 1/2"; D: 11 1/2"

Weight: 17.6 lb

FOR/FOA SYDNEY: TS 500, \$491.00; PS 500 AC, \$98.00

CONSULT YOUR LOCAL RADIO DEALER, OR

MAIL THIS COUPON *today*

Please forward free illustrated literature and specifications on Trio equipment.

Name.....

Address.....



(A unit of Jacoby Mitchell Holdings Ltd.)
376 EASTERN VALLEY WAY, ROSEVILLE, N.S.W.,
Cables and Telegraphic Address: 'WESTELEC',
Sydney. Phone: 40 1212

LOW DRIFT CRYSTALS



1.6 Mc. to 10 Mc.,
0.005% Tolerance, \$5



10 Mc. to 18 Mc.,
0.005% Tolerance, \$6



Regrinds \$3

THESE PRICES ARE SUBJECT
TO SALES TAX

SPECIAL CRYSTALS:
PRICES
ON APPLICATION

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY, E.7,
VICTORIA

Phone 83-5090

LOG BOOK

IS NOW AVAILABLE

Larger, spiral-bound pages
with more writing space.

Price 75c each

plus 17 Cents Post and Wrapping

Obtainable from your Divisional
Secretary, or W.I.A., P.O. Box 36,
East Melbourne, C.2, Victoria.

DURALUMIN, ALUMINIUM ALLOY TUBING

IDEAL FOR BEAM AERIALS AND T.V.

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS— $\frac{1}{4}$ " TO 3"

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

GUNNERSSEN ALLEN METALS PTY. LTD.

SALMON STREET,
PORT MELBOURNE, VIC.

Phone: 64-3351 (10 lines)
Telegrams: "Metals," Melb.



HANSON ROAD,
WINGFIELD, S.A.

Phone: 45-6021 (4 lines)
Telegrams: "Metals," Adel.

CALL BOOK

1968-69 EDITION

NOW AVAILABLE!

75 Cents, from your usual Supplier

*AEGIS

*Registered Trade Mark

INSTRUMENT KNOBS

*Just 4 of our
wide range of
bakelite and metal
knobs*



MV3/R

Black with silver insert,
brass bush bored for $\frac{1}{4}$ "
shaft and 2 grub screws
at 90°, $\frac{1}{8}$ " diam. x $\frac{3}{8}$ "
high.

Available
everywhere.
Write for
detailed,
illustrated
leaflet
and prices

AEGIS PTY. LTD.



MK 132

Metal knob, gold,
plain, 1 grub screw.
 $\frac{1}{4}$ " diam. x 1" high.



MK 231

Metal knob, silver,
knurled black ring
and black vertical
line, 2 grub screws
at 90°, $\frac{15}{16}$ " diam.
x $1\frac{1}{2}$ " high.



MK 144

Metal knob, silver,
silver knurling with
one black vertical
line, one grub screw.
 $\frac{15}{16}$ " diam.
x $\frac{13}{16}$ " high.

347 Darebin Rd., Thornbury, Vic., 3071.
P.O. BOX 49 Thornbury, Vic., 3071
Phones: 49 1017, 49 6792

AEGIS KNOBS LEAFLET

A recent addition to the range of Aegis technical leaflets is a data and specification sheet of a wide variety of instrument knobs to suit a number of equipment applications. Availability is free from Aegis Pty. Ltd., 347 Darebin Road, Thornbury, Vic., 3071, or through their interstate agents: N.S.W.: Watkin Wynne Pty. Ltd.; S.A.: Neil Muller Pty. Ltd., and Qld.: P. H. Phillips Pty. Ltd.

V.H.F. U.H.F.

Interested in what European Amateurs are accomplishing on these bands. Commencing January 1969, the authoritative German v.h.f. u.h.f. magazine UKW-Berichte will be published quarterly in English. 60 pages of the latest techniques, detailed construction articles on v.h.f. u.h.f. gear and antenna written by top Amateurs in Europe.

Annual subscription \$5.50 AIR MAILED direct from the German publishers. Send a cheque/money order to the Australasian representative of UKW-Berichte, G. Clarke, VK-2ZXD, 2 Beaconsview St., Balgowlah, N.S.W., 2093.

A LIMITED number of sample copies of the German edition are available free for inspection.

ATTENTION VK5's

**ELIZABETH SURPLUS
SUPPLIES**
(newly opened)

offers you Disposals Equipment at Lower Prices

OPEN ALL DAY SATURDAY

Elizabeth Surplus Supplies

**TRIMMER ROAD,
ELIZABETH SOUTH, S.A.**

BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY
AND OUTPUT



Our Crystals cover all types and frequencies in common use and include overtone, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, B7G, Octal, HC-18U.

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE AVAILABLE IN FT243 HOLDERS:

6280, 4095, 4535, 2760, 2524 Kc.
5,500 Kc. T.V. Sweep Generator Crystals, \$7.25;
100 Kc. and 1000 Kc. Frequency Standard, \$17;
plus Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on application.

455 Kc. Filter Crystals, vacuum mounted, \$13 each plus Sales Tax.

ALSO AMATEUR TYPE CRYSTALS—3.5 Mc. AND 7 Mc. BAND.

Commercial—0.02% \$7.25, 0.01% \$7.55, plus Sales Tax.

Amateur—from \$6 each, plus Sales Tax.

Regrinds—Amateur \$3, Commercial \$3.75.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carrell, Box 2102, Auckland.
Contractors to Federal and State Government Departments.

BRIGHT STAR RADIO

LOT 6, EILEEN ROAD, CLAYTON, VIC.

Phone 546-5076

With the co-operation of our overseas associates our crystal manufacturing methods are the latest.



- * Swan 350C, five-band a.m.c.w.-s.s.b. Transceiver, \$547.
- * Swan 500C, five-band a.m.c.w.-s.s.b. Transceiver, \$670.
- * Swan TV-2, 2 mx Transverter, \$384.10.
- * Swan 250, 6 mx Transceiver, \$433.
- * Swan 230X 240v. a.c. Power Supply with speaker in matching cabinet, \$115.
- * Swan 410C External VFO, five-band, Transistorised, \$180.
- * Swan VX2 plug-in VOX Unit, \$53.
- * Swan 22 Adaptor for External VFO, \$42.
- * Model 45 Swantenna five-band Mobile Whip Antenna, \$130, manual.
- * Model 55 Swantenna five-band Mobile remote control Whip Antenna, \$190.
- * WFS500 12v. DC 500 watt Mobile Power Supply, \$150.
- * Swan spare parts and warranty service.

OTHER EQUIPMENT

- * Hallicrafters Transmitters and Receivers.
- * TRIO JR60U five-band Receiver, \$277.
- * TRIO JR200 four-band Receiver, \$136.
- * TRIO 9R59DE four-band Receiver, \$175.
- * TRIO JR500SE seven-band Receiver, \$293.50.
- * TRIO TR2E 144 Mc. Transceiver, 25 watts, \$276.
- * TRIO TS500 seven-band Ham Transceiver, \$480.
- * TRIO PS500 AC Power Supply and speaker for TS500, \$96.
- * Yaesu SSB Equipment.
- * Pearce-Simpson Marine Radio Telephones.
- * Sceptre Depth Sounders, \$69.
- * Hy-gain, Mosley, and W.F.S. Beams.
- * W.F.S. Quads.
- * B. & W. Switches.
- * Dow Key Relays.
- * Petrol and Diesel powered Generating Sets in AC and DC to requirements.

W.F.S. ELECTRONICS SUPPLY CO.

227 VICTORIA ROAD,
RYDALMERE, N.S.W.

Phones: 638-1715, 638-1355

ATLANTIC RADIO

14 Glebe St., Edgecliff, N.S.W.
Phone 32-5465

Get . . . MAXIMUM SIGNAL transfer, with minimum power loss!



USE FORMULA III., "LO-LOSS" OPEN WIRE TRANSMISSION LINE

- * DESIGNED FOR UHF-VHF OPERATION.
- * SOLID COPPER CONDUCTOR
- * CONSTANT 300 OHM IMPEDANCE
- * POLYTHENE SPACERS
- * USED BY SERVICES AND GOVT. DEPTS.

Formula III. Aerial Feeder compared with ribbon in db's per 100 ft., at 100 Mc.:

		WET	DRY
Formula III. Aerial Feeder ..	300Ω	1.2	0.4
Flat Ribbon ..	300Ω	7.6	1.5

USE GENUINE "LO-LOSS" STAND-OFF INSULATORS

Available from electrical and radio parts wholesalers

Australian Manufacturer:

E. W. CORNELIUS PTY. LTD.

182 BAY STREET, BRIGHTON, VIC., 3186

Phone 96-3232



Changes for Mobile Radiotelephone Services

Licencees of V.H.F. land and harbour mobile radiotelephone services, now operating in 30 kc/s channelling areas, are advised that if they have not already installed equipment which meets the Australian Post Office 30 kc/s channelling specification, they must do so before 30 June, 1969.

This requirement has been brought about by the growing demand for V.H.F. mobile radiotelephone services in city areas which is taxing the existing channels available. The change to 30 kc/s channelling will enable more radiotelephone services to be brought into operation as they are required.

However, some changes to existing equipment will be necessary and the following programme for conversion, which is designed to cause the least inconvenience to all concerned, has been adopted:—

As from 30 June, 1969, licencees of V.H.F. mobile radiotelephone services operating in 30 kc/s channelling areas within the frequency bands 70-85 Mc/s and 156-174 Mc/s* will be required to make necessary changes so that:—

- (i) All base station transmitter/receivers (both amplitude and angle modulated) employed in a base station installation shall be of a type complying with the relative Post Office specification and approved for 30 kc/s operation and shall be operated in accordance with the terms of that specification.
- (ii) All angle modulated mobile transmitters shall be adjusted to function with a maximum deviation of ± 5 kc/s.

* This excludes the International Maritime Mobile V.H.F. Radiotelephone and the existing Australian Post Office Subscriber Services.

Early conversion will assist manufacturers in meeting delivery dates for equipment.

**FURTHER DETAILS MAY BE OBTAINED FROM THE SUPERINTENDENT,
RADIO BRANCH, G.P.O., IN YOUR CAPITAL CITY.**

AUSTRALIAN POST OFFICE

INDEX TO VOLUME 36-1968

ANTENNAE

A New Field-Day V.H.F. Beam	Oct. p.17
Further Data on the Single Loop Triband Cubical	Sep. p.8
Simplified Antenna Switching for H.F. Bands	May p.12
Single Loop Triband Cubical Quad Element	Apr. p.3
Some Thoughts on "V-V" Beams for 14 and 21 Mc.	Jun. p.12
The "Reed Rhombus"—A Low Angle Antenna	Oct. p.21
"The World with a Triangle"	Oct. p.11

AUDIO AND MODULATORS

Speech Compression for Exciters	Apr. p.13
Three-Transistor Audio Compressor	Jan. p.9

CONTEST RULES AND RESULTS

Australasian Results of 1967 A.R.R.L. DX Test	Mar. p.20
National Field Day Contest: 1968 Results	Jun. p.11
Oceania Results of 1967 "CQ" S.S.B. Contest	Mar. p.20
Oceania Winners, 8th All Asian DX Contest, 1967	Aug. p.13
Remembrance Day Contest: 1968 Rules	Jul. p.12
1968 Results	Nov. p.10
Ross Hull Memorial Contest: 1967-68 Results	May p.15
1968-69 Rules	Dec. p.10
Victorian 160 Metre Contest	Sep. p.11
VK-ZL-Oceania DX Contest: 1967 Results	Apr. p.15
1967 Results, Late Entries	May p.15
1968 Rules	Aug. p.13

INSTRUMENTS

A Field Effect Transistor Voltmeter	Aug. p.11
Simple Multipurpose Square Wave Generator	Sep. p.7
Simple Step Attenuator	Jan. p.4
S.W.R. Indicators—Fact or Fiction	Jul. p.9
The Millimatch	Jan. p.6

MISCELLANEOUS

Antennas and Animals	Oct. p.23
Aus. DX Century Club Award	Jan. p.11
Aus. D.X.C.C. Countries List	Jan. p.12
Aus. S.W.L. Cent. Club Award	Jan. p.16
Aus. V.H.F. Cent. Club Award	Jan. p.11
Back Numbers of "A.R."	Jan. p.15
Change in Radio System for Low Powered M.F. and H.F. Radiotelephone Services	Jan. p.7
Field Day Fun—or—Heat, Flies and Donga	Sep. p.12
Heard All VK Call Areas S.W.L. Award	Feb. p.19
Important Rules Change for W.I.A. W.A.S. Ward	Jun. p.14
Intruder Watch	Oct. p.24

Moon-Bounce Schedule	Apr. p.16
Morse Code Proficiency	Jun. p.13
New Supra High Frequency Record Claimed	Apr. p.9
Presentation of Merit Award to VK3ATN	Apr. p.22
State Intruder Watch Coordinators	Dec. p.18
The New Handbook	Jan. p.18
Ditto	Feb. p.15
The Remembrance Day Formula	Aug. p.15
V.H.F./U.H.F. State Records, March 1968	May p.20
Vic. National Parks Award	Feb. p.20
Ditto	May p.22
W.I.A. Federal Executive Balance Sheet	May p.19
W.I.A. Federal President's Report	May p.16
W.I.A. Secures Morse Speed Reduction	Feb. p.2
Worked All VK Call Areas (W.A.V.K.C.A.) Award	Oct. p.27
World Administrative Space Radio Communications Conference	Dec. p.16
"XL" Operator Club	Mar. p.20

POWER SUPPLIES

Additional Notes on Transistor Regulated Power Supplies	Apr. p.10
Handy D.C. Supply for the Bench	Apr. p.7
Mobile Power Supply	Feb. p.9
Mobile Power Supply for a Galaxy III	Jan. p.5
Sidac—A Poor Man's Variac	Aug. p.9
Simple Low Cost High Voltage Supply	Mar. p.9
Errata	Sep. p.10
Technical Correspondence: Handy D.C. Supply for the Bench	Jul. p.8

RECEIVERS

Adapting the Geloso G209 for S.S.B. Reception	Jul. p.8
An All FET 2 Mx Converter	Jul. p.5
Improving the Signal-to-Noise Ratio of Receivers	May p.12
Integrated Circuit I.F. Strip	Sep. p.8
Project—Solid State Transcvr.: Part One	Nov. p.13
Part Two	Dec. p.7
Ring Modulator-Detector	Jan. p.8
Simple and Easy to Build Product Detector	Jul. p.6
Simple High Performance 6 Metre Converter	Oct. p.20
Solid-State Modules: Part One—For Valve Replacement in Com. Rx's	Jun. p.8
Part Two—Transistorising a BC454	Jun. p.10
Table Top S.S.B. Transceiver for Six Metres	Sep. p.4
Errata	Nov. p.11
Transist. Radio Noise Limiter	Apr. p.9
Transverter for 21 or 28 Mc.	Dec. p.6

Using the MR3 Carphone on A.C.	Mar. p.14
VK3 V.H.F. Group 6 Metre Converter—Untuned Output	Jul. p.14

TECHNICAL MISCELLANEOUS

An Introduction to the Field Effect Transistor	May p.6
Aus. Oscar 'A'—Users' Guide: Part One	Feb. p.3
Part Two	Mar. p.10
FT241 Crystals—Channel Nos. 0 to 79 and 270 to 375	Nov. p.8
Hints and Kinks: Transceiver Relays	Nov. p.20
Project Australis Hi-Bal.	May p.14
Radio Automatic Teletype Made Easy	May p.10
Repeater Technical Group Meeting	Nov. p.17
Single Sideband Transceiver Development in Australia	Sep. p.9
The Unijunction Transistor	Mar. p.2
Tinned Fuse Wire—Fusing Current and Time Values	Jan. p.9
Using a Phase Comparator	Apr. p.12
When Are They Biting?	Oct. p.13
40 Metre D.F. Rod with Transistor Pre-amplifier	Sep. p.6

TRANSMITTERS

Crystal Locked A.M.-C.W. Transmitter for 6 Metres	Jun. p.6
Errata	Jul. p.14
"Das Softenboomer 160": A Low Cost Rig for 160 Metres	Mar. p.5
Low Power Two Metre S.S.B. Transmitter	Jan. p.3
Project—Solid State Transcvr.: Part One	Nov. p.13
Part Two	Dec. p.7
Ring Modulator-Detector	Jan. p.8
Sidebanding—by a Greybeard for Greybeards	Aug. p.8
Small 150W. A.M.-C.W. Transmitter using a 6DQ5 Final	Aug. p.6
Speech Compression for Exciters	Apr. p.13
S.S.B.: Asymmetrical Crystal Filters	May p.9
S.S.B. Transmitter—An Amateur Engineering Project: Part One	Oct. p.6
Part Two	Nov. p.6
Part Three	Dec. p.11
Table Top S.S.B. Transceiver for Six Metres	Sep. p.4
Errata	Nov. p.11
Technical Correspondence: Transistor Overtone Crystal Oscillator	Mar. p.15
The Shoebox II. Linear	Feb. p.7
The Stability of Transistor Variable Freq. Oscillators	Feb. p.11
Trade Review: FL-50 S.S.B. Transmitter	Oct. p.14
Transistor Sideband—C.W.	Jul. p.7
Transverter for 21 or 28 Mc.	Dec. p.6
Using the MR3 Carphone on A.C.	Mar. p.14

A LARGE RANGE OF TRANSMITTERS, RECEIVERS, TEST GEAR, AND DISPOSALS RADIO PARTS AVAILABLE

● CRYSTAL CALIBRATOR No. 10

Nominal Frequency Range: 550 Kc. to 30 Mc.
Internal 500 Kc. crystal. VFO frequency coverage: 250-500 Kc. 2 Kc. dial divisions.

Used (good condition): **\$10.50.**

New (sealed cartons): **\$13.00.**

Packing and freight: \$1.50.

● MILLER 8903B PRE-WIRED I.F. STRIPS

455 Kc. centre frequency, 55 db. gain. Employs two PNP transistors and diode detector.

Price **\$9.50.**

● EICO 753 TRI-BAND S.S.B. TRANSCEIVER

Full CW-AM-SSB coverage, 80-40-20 metres. 180w. PEP SSB-CW. VOX-PTT-ALC. 10 Kc. Receiver offset tuning.

Kit **\$328.78**, Wired **\$428.78.**

WANTED TO BUY

Communication Receivers, Test Equipment, etc. Call, write or phone. Equipment inspected and picked up at your convenience any night or week-end.

● VALVE SPECIALS

807—70 cents ea.

815—70 cents ea.

6AC7—20 cents ea. or 12 for \$2.

6J6—30 cents ea. or 7 for \$2.

6CQ6—20 cents ea. or 6 for \$1.

VR150/30—75 cents ea. or 3 for \$2.

VR105/30—75 cents ea. or 3 for \$2.

QB2/250 (813)—\$7 ea.

TZ40—75 cents ea.

6H6 (Metal)—20 cents ea.

DM71 (Indicator Tube)—40c ea. or 6 for \$2.

● TRANSISTORS

2SC73

2SD65

2T65

2T76

OC66

All at Bargain Price of **25 cents each.**

● STAR SR700 SSB AMATEUR BAND RECEIVER

Frequency coverage: 3.4-29.7 Mc. in 7 bands. Triple conversion, employs xtal locked 1st and 3rd conversion oscillators. Selectable USB or LSB. Selectivity variable, 0.5 Kc. to 4 Kc. 1 Kc. dial calibration. Three stages double locked geared dial mechanism, 30 Kc. per turn tuning rate. Vackar oscillator employed in VFO for maximum stability.

Price **\$461.50.**

● A111 9 Mc. SSB EXCITER

A fibre-glass printed circuit board, the finest German crystal filter, diode ring modulator, and solid state circuitry all contribute to make the A111 the finest SSB Exciter available. Specifications: Sideband suppression, 80 db.; carrier sup., 65 db.; audio freq. response, 350 to 3,000 cycles; mic. input, 1 mV. on 5K ohm load. Incorporates VOX amplifier and relay amplifier.

Price with KVG XF9B Filter, **\$120.**

● A112 5 Mc. VFO

Frequency coverage: 4950 to 5550 Kc. Frequency stability better than 100 c/s. over 12 hours long term; better than 8 c/s. over 10 minutes if enclosed in suitable box. Output: 350 mV. on 220 ohm load.

Price **\$22.**

ALL ITEMS FREIGHT EXTRA

UNITED TRADE SALES PTY. LTD.


280 LONSDALE ST., MELBOURNE, VIC. (Opp. Myers)

Phone 32-3815



Yaesu SSB EQUIPMENT

for Amateur Radio Communication

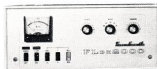

FLDX-2000 Linear Amp.
80-10 mx, AB2 G.G.



SP-400
Speaker



FRDX-400 Receiver
160-2 mx, WWV, C.B.



FLDX-400 Transmitter
80-10 mx, peak in. 300w.



FTDX-400 Transceiver
80-10 mx, peak inp. 500w.




FTDX-100 Transceiver
80-10 mx, Transistorised, 150w.




FT-50 Transceiver FV-50 V.F.O.
80-10 mx, peak inp. 100w.



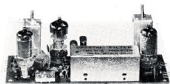FF-30DX 3-Section L.P. Filter
For T.V.I. reduction



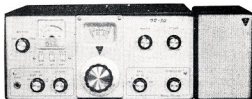Type "F" S.S.B. Generator
Basis for Tx Construction



FR-50 Receiver SP-50
80-10 mx, WWV Speaker



FL-50 Transmitter FV-50 V.F.O.
80-10 mx, peak inp. 125w.

Australian Agents:

BAIL ELECTRONIC SERVICES

60 SHANNON ST., BOX HILL NTH., VIC., 3129

Phone 89-2213

Rep. in N.S.W.:

A. J. BRUCESMITH

47 HYMAN ST., TAMWORTH, N.S.W., 2340

Phone (STD 067) 66-1010